

Computer-Aided VLSI System Design


Chapter 6. Static Timing Analysis (STA)

Lecturer: Chun-Wei Chang

Graduate Institute of Electronics Engineering, National Taiwan University




NTU GIEE

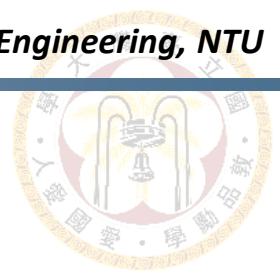


Outline

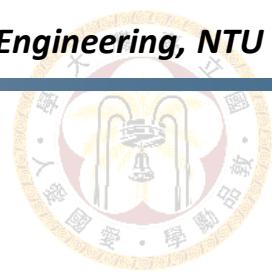
- **Introduction**
- **Static Timing Analysis**
- **Environment Setting**
- **Special Timing Paths**



Timing Analysis

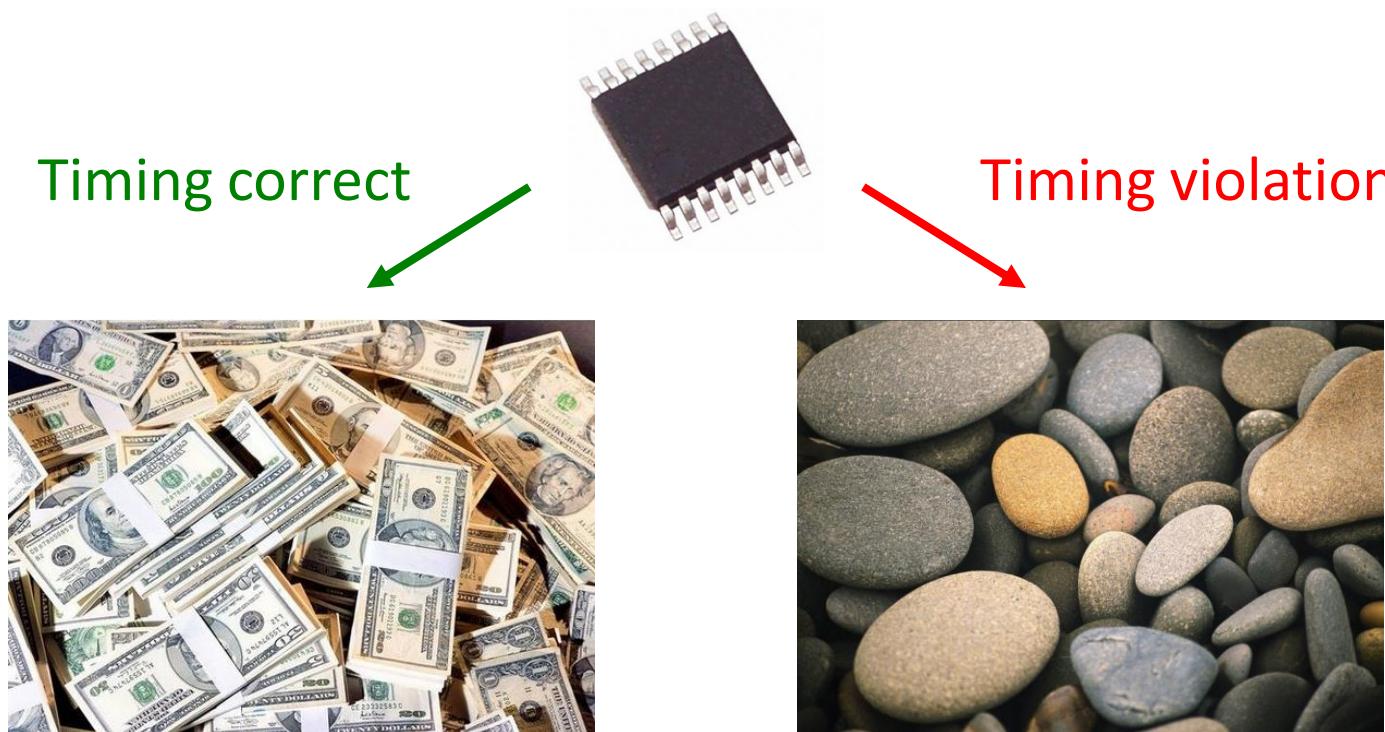
- Timing analysis is an integral part of ASIC/VLSI design flow
 - Especially for synchronous design
- The design will not work if it fails the timing analysis



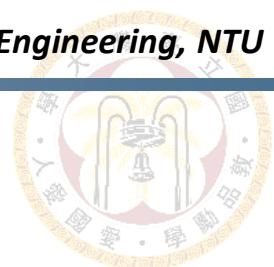


The Goal of Timing Analysis

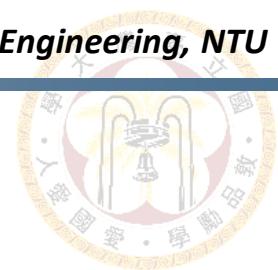- **To assure all signals will arrive neither too early nor too late**
 - **Too early:** hold violation
 - **Too late:** setup violation
- **If there are timing violations**
 1. Check the simulation environment and settings
 2. Modify the settings of synthesis tools
 3. Fix your design architecture




Dynamic Timing Analysis (DTA)

- **Also called Testbench Simulation**
 - Test vectors are applied during the simulation time
 - Simulator calculates both the logic values and delays
- **Disadvantages**
 - Virtually impossible to do exhaustive analysis
 - Vector creation takes too long
 - Incomplete timing coverage
 - Hard to identify the cause of failure because the function and timing are analyzed at the same time
 - Requires more memory and CPU resources
 - Huge analysis space
 - Long simulation time

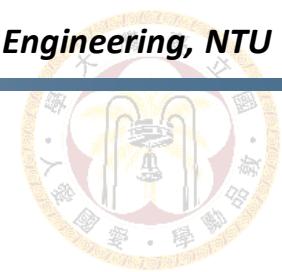



Static Timing Analysis (STA)

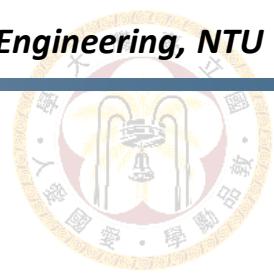- An **exhaustive** verification of all timing checks
- Analyzes every timing path according to the given constraints
- No need for circuit simulation
 - Less memory and CPU resources than DTA
- Disadvantages
 - For synchronous logic only
 - Tricky constraints beyond the boundaries of single clock flip-flop design chips:
 - False paths
 - Multicycle paths
 - Multiple clock domains




When to Perform STA

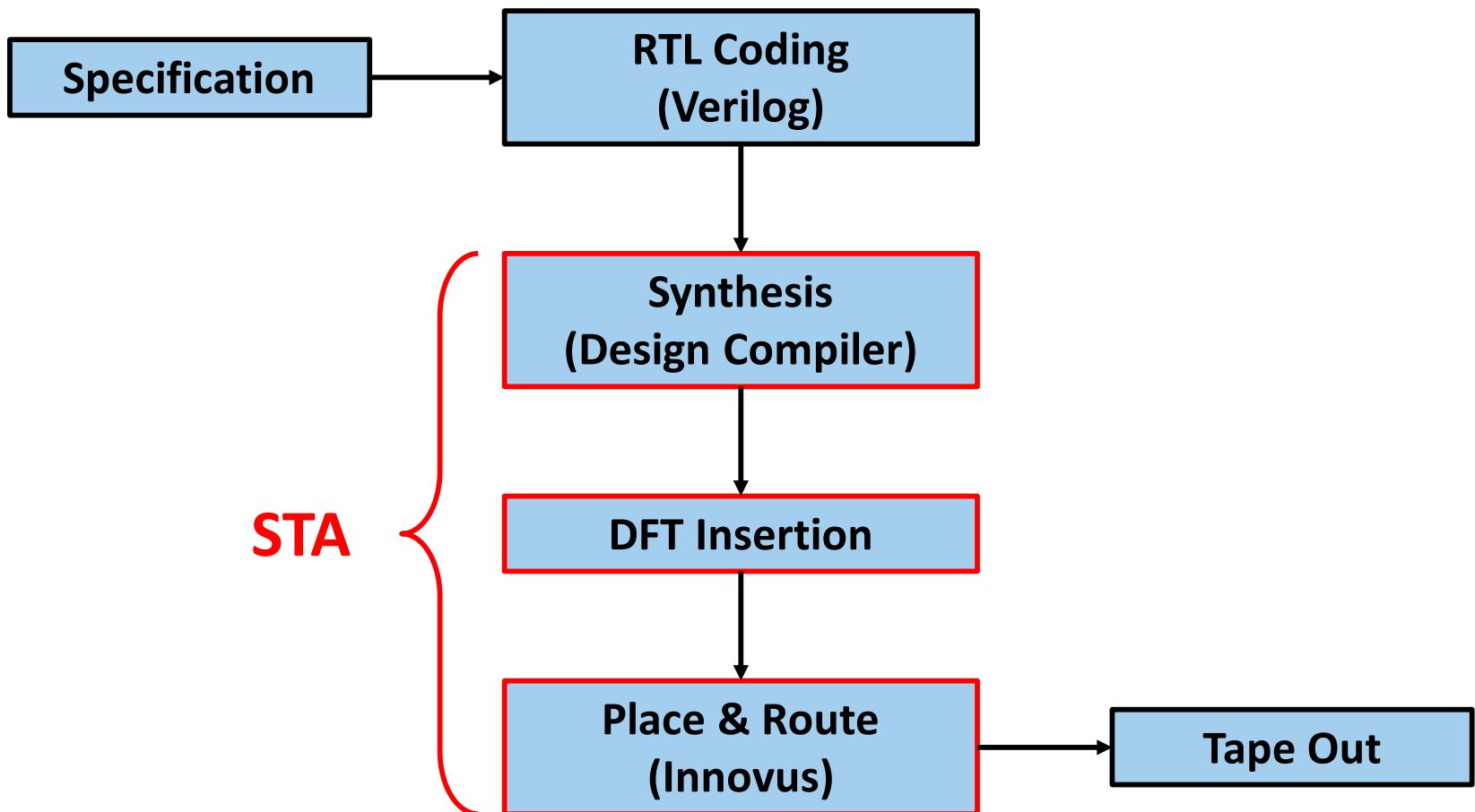

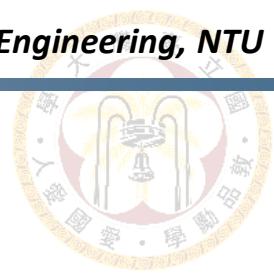


Outline

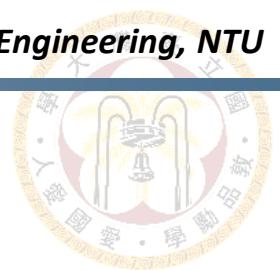
- Introduction
- **Static Timing Analysis**
- Environment Setting
- Special Timing Paths



Steps of STA

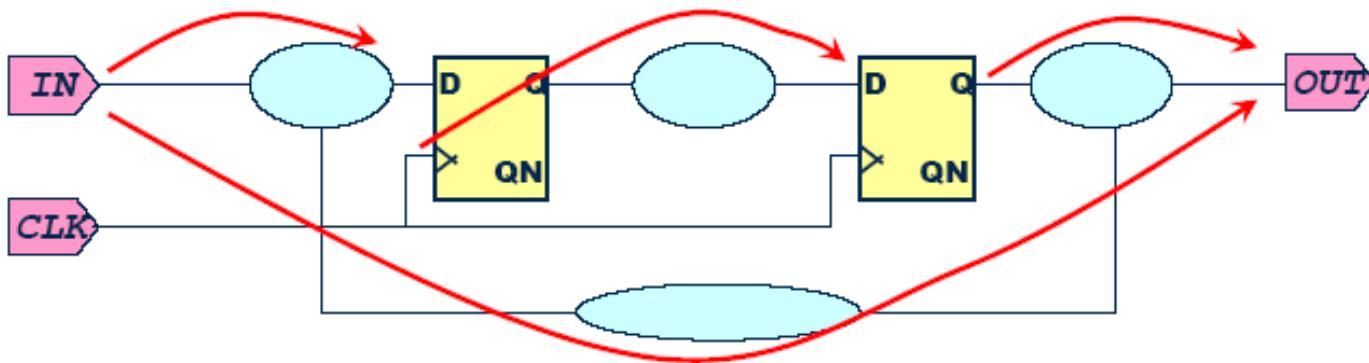
1. Break the design into a set of timing paths
2. Calculate arrival time and required time of each path
3. Calculate the slack of each path




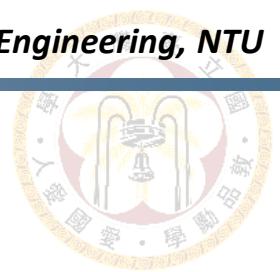


Steps of STA

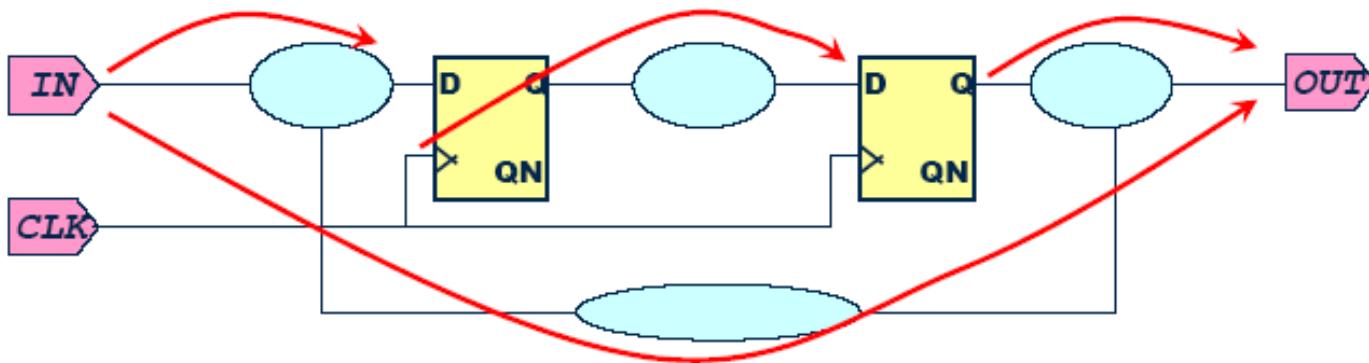1. Break the design into a set of timing paths
2. Calculate arrival time and required time of each path
3. Calculate the slack of each path



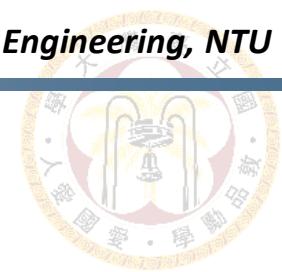


Four Types of Timing Paths

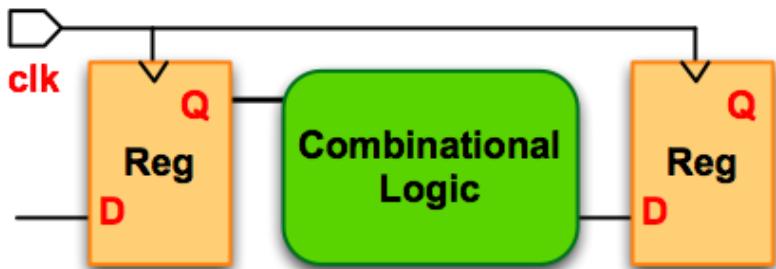

Register-to-register (reg2reg)

Start Point: clock pin of sequential device

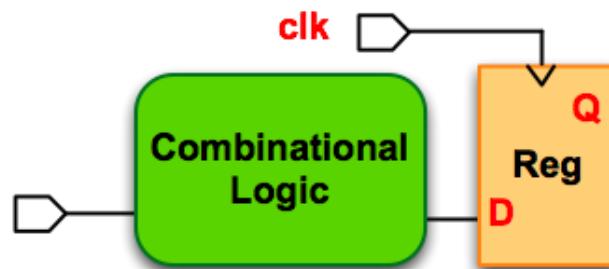
End point: data input pin of sequential devices



Input-to-register (in2reg)

Start Point: primary input port

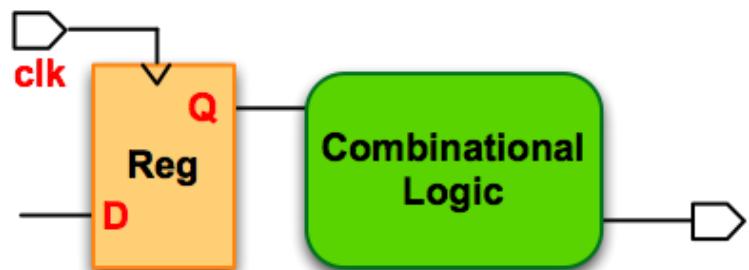End point: data input pin of sequential devices



Register-to-output (reg2out)

Start Point: clock pin of sequential device


End point: primary output port



Input-to-output (in2out)


Start Point: primary input port


End point: primary output port

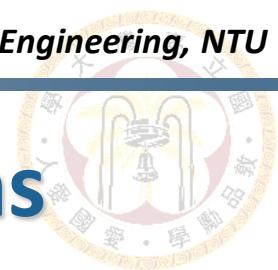

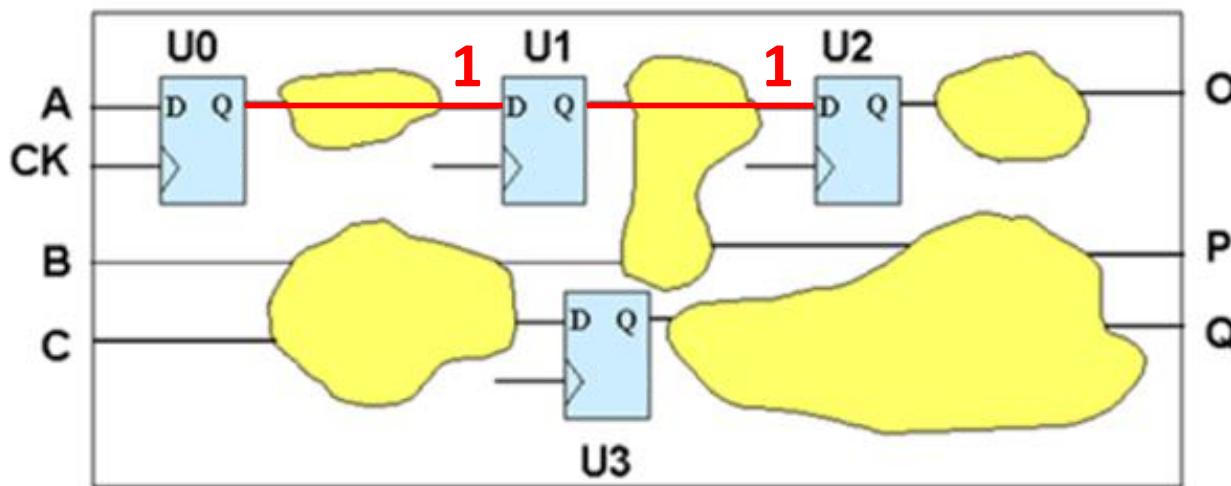Example: Register-to-Register Paths


- How many register-to-register paths are there in this design?
 - 2




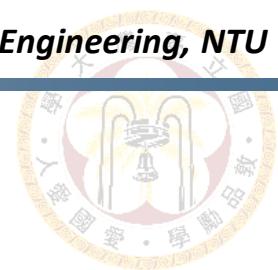

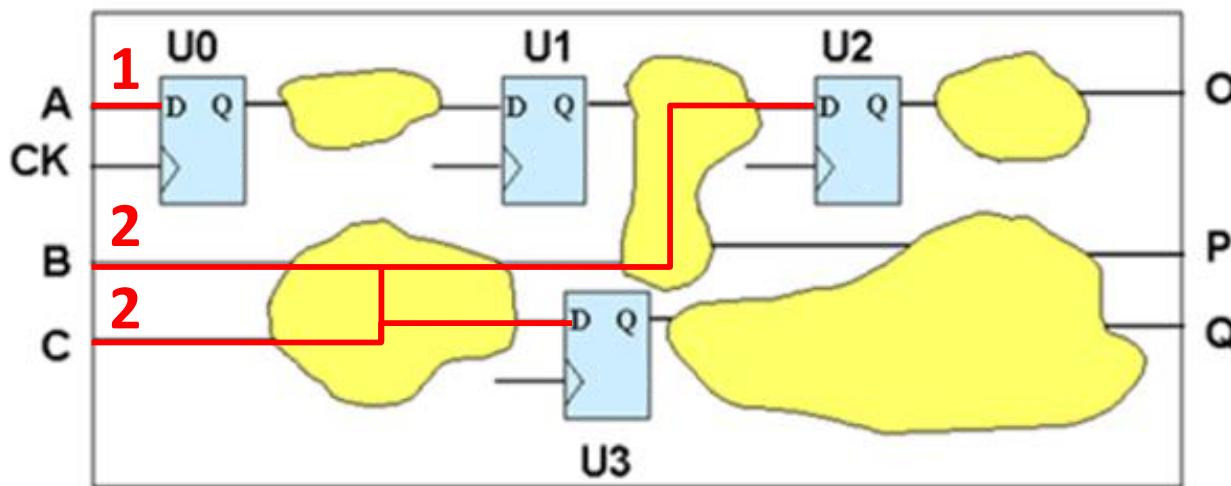Example: Input-to-Register Paths


- How many input-to-register paths are there in this design?
 - 5




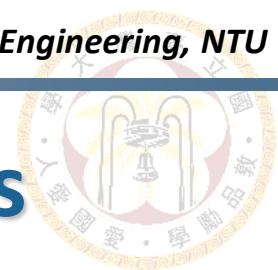

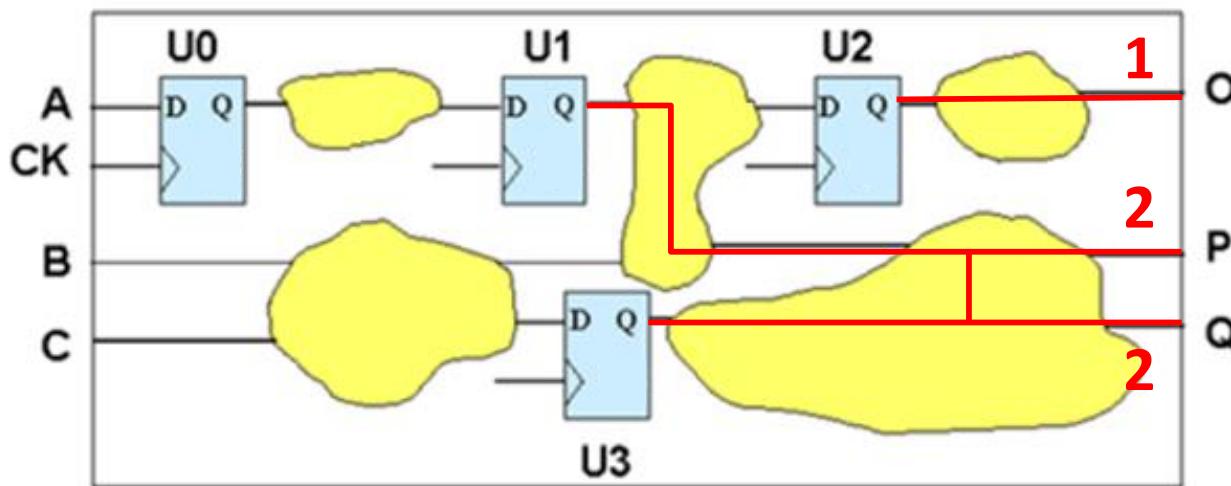Example: Register-to-Output Paths


- How many register-to-output paths are there in this design?
 - 5




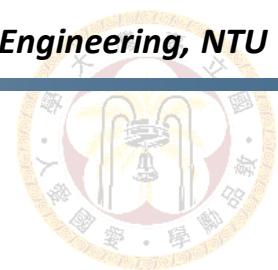

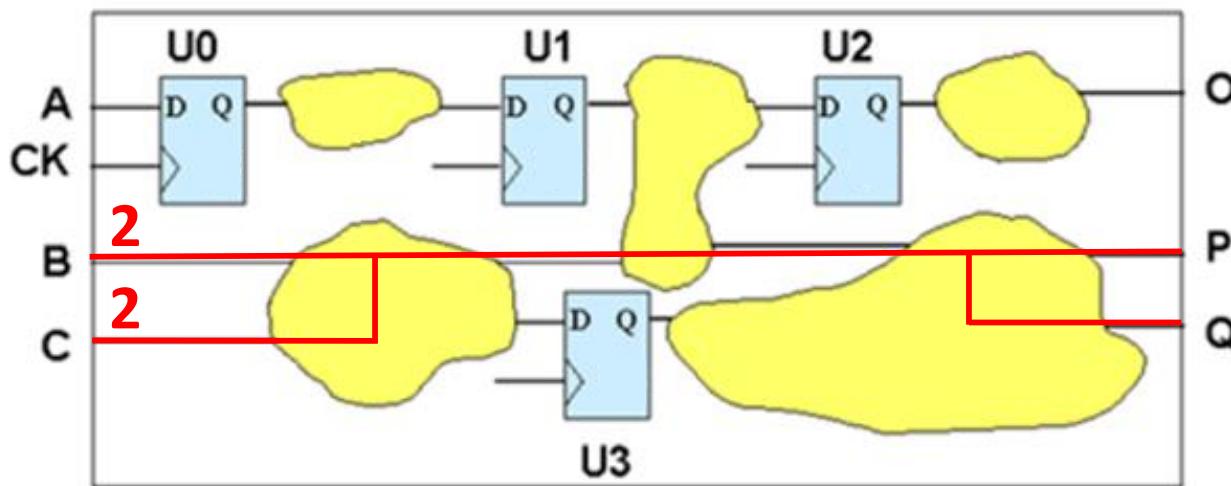Example: Input-to-Output Paths


- How many input-to-output paths are there in this design?
 - 4




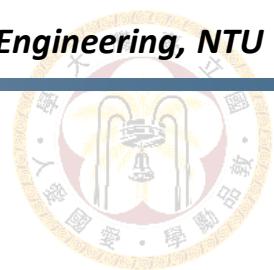

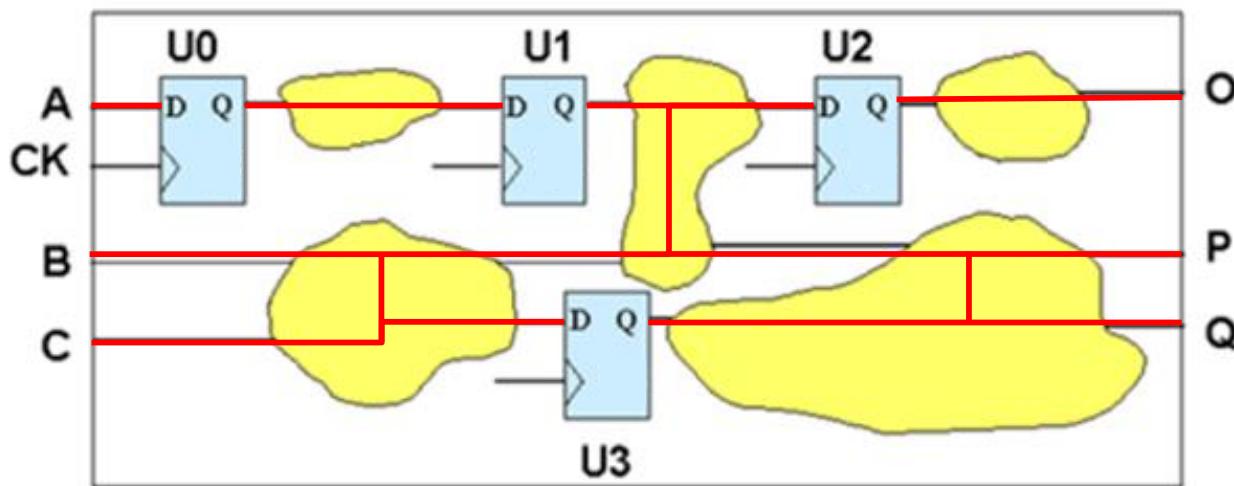Example: Timing Paths


- How many timing paths are there in this design?
 - $2 + 5 + 5 + 4 = 16$




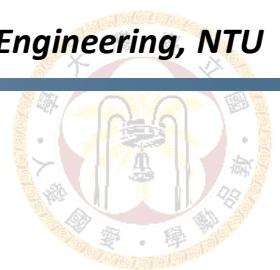


Steps of STA

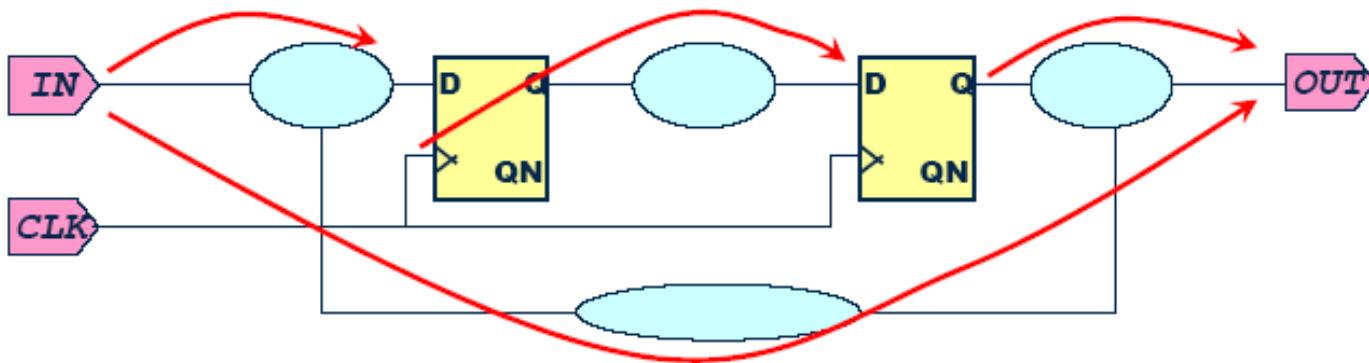1. Break the design into a set of timing paths
2. Calculate arrival time and required time of each path
3. Calculate the slack of each path




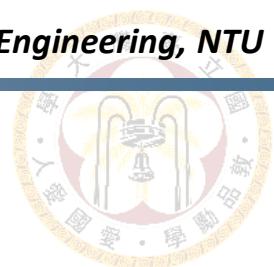


Setup Time & Hold Time

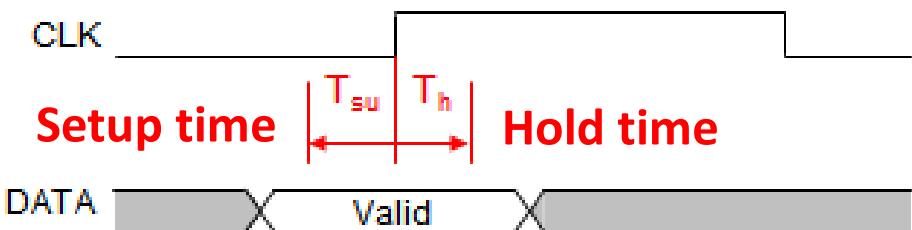

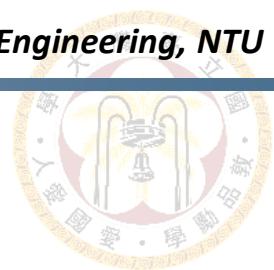- **Setup Time T_{su}**
 - The minimum amount of time before the clock's active edge that the data must be stable
 - Violation may cause incorrect data to be captured
- **Hold Time T_h**
 - The minimum amount of time after the clock's active edge during which data must be stable
 - Violation may cause incorrect data to be latched




Setup Check (Ideal CLK)

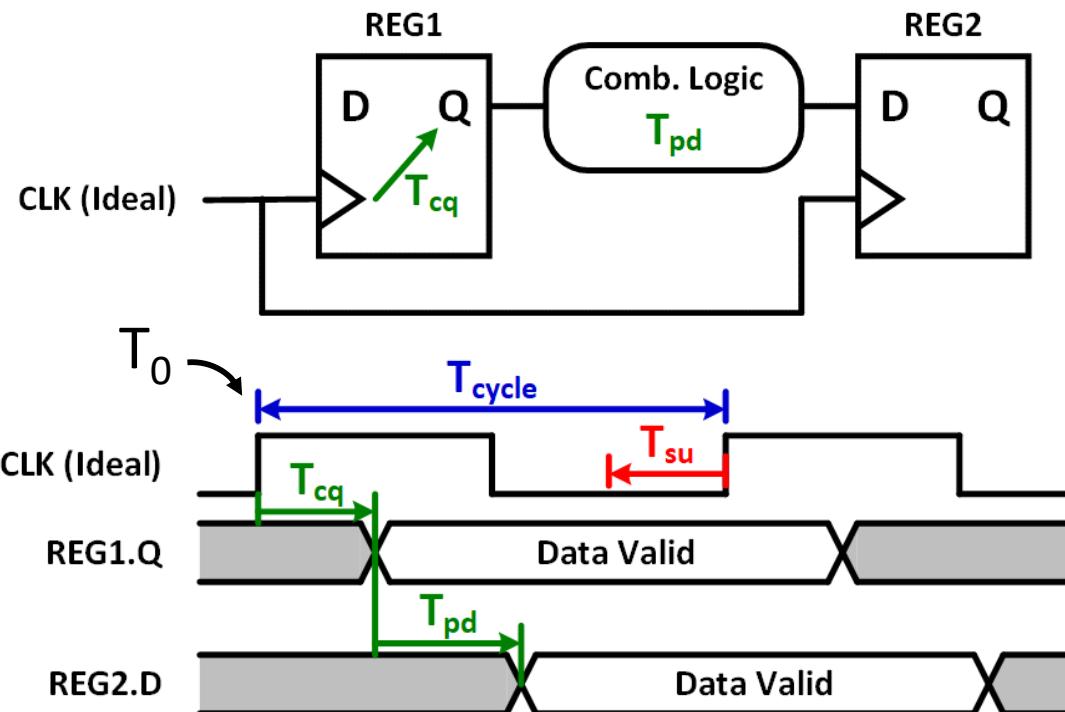


Arrival time (AT): $T_0 + T_{cq} + T_{pd}$

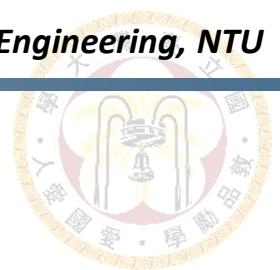
Required time (RT): $T_0 + T_{cycle} - T_{su}$



Hold Check (Ideal CLK)

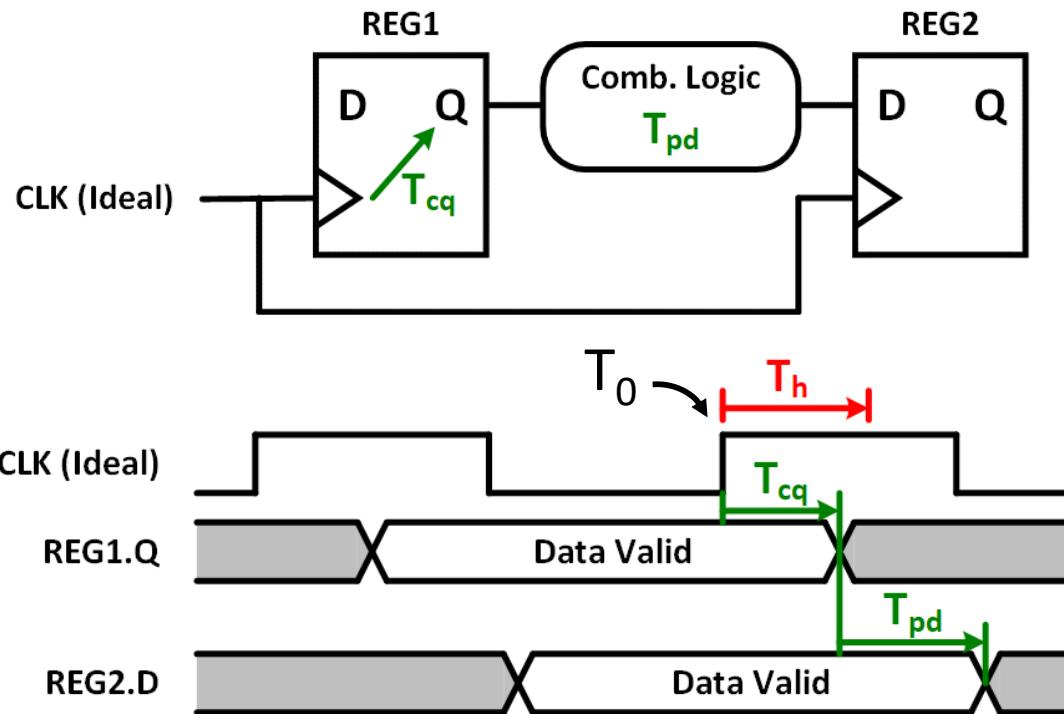


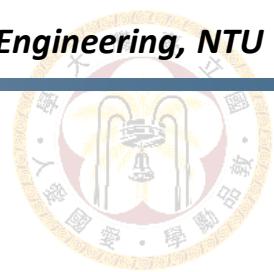
Arrival time (AT): $T_0 + T_{cq} + T_{pd}$
Required time (RT): $T_0 + T_h$



Clock Latency

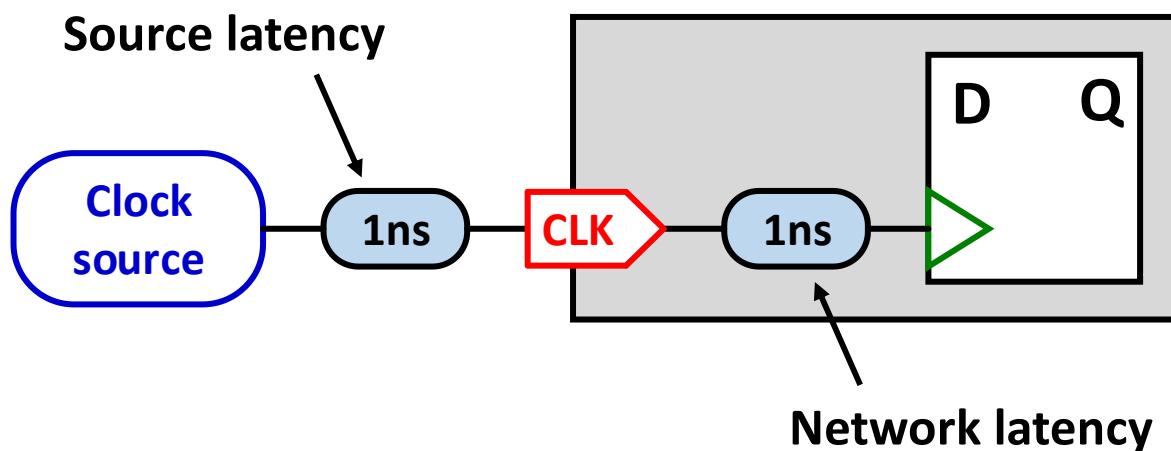
- **Source latency**
 - Delay from the **clock source** to the **clock definition point (CLK)**
- **Network latency**
 - Delay from the **clock definition point (CLK)** to the **clock pin of a sequential cell**




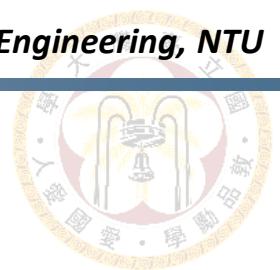

Clock Uncertainty: Skew

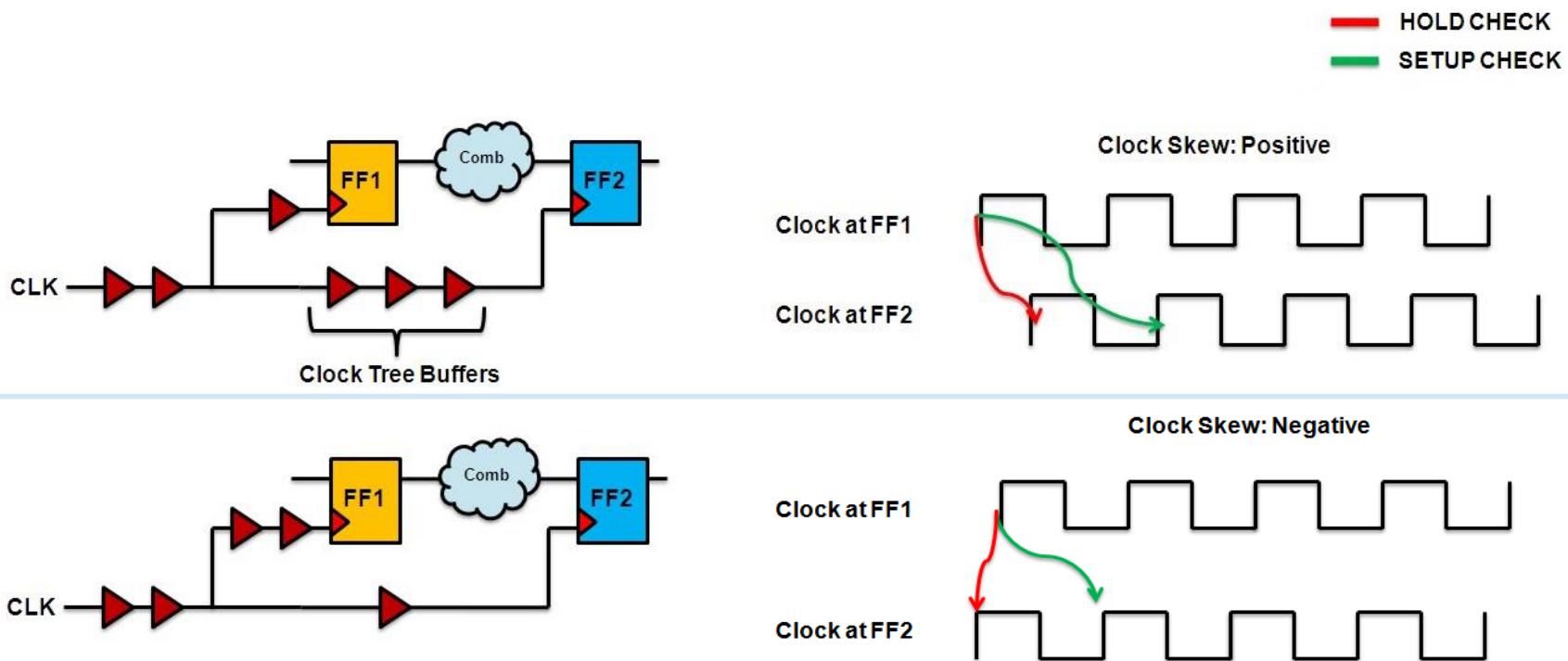
- The difference in arrival time of a clock transition on an integrated circuit



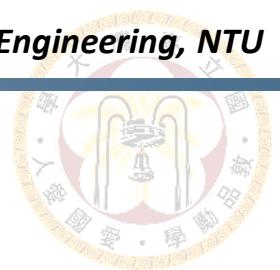


Setup Check: Arrival Time

- Consider the same circuits in p. 19

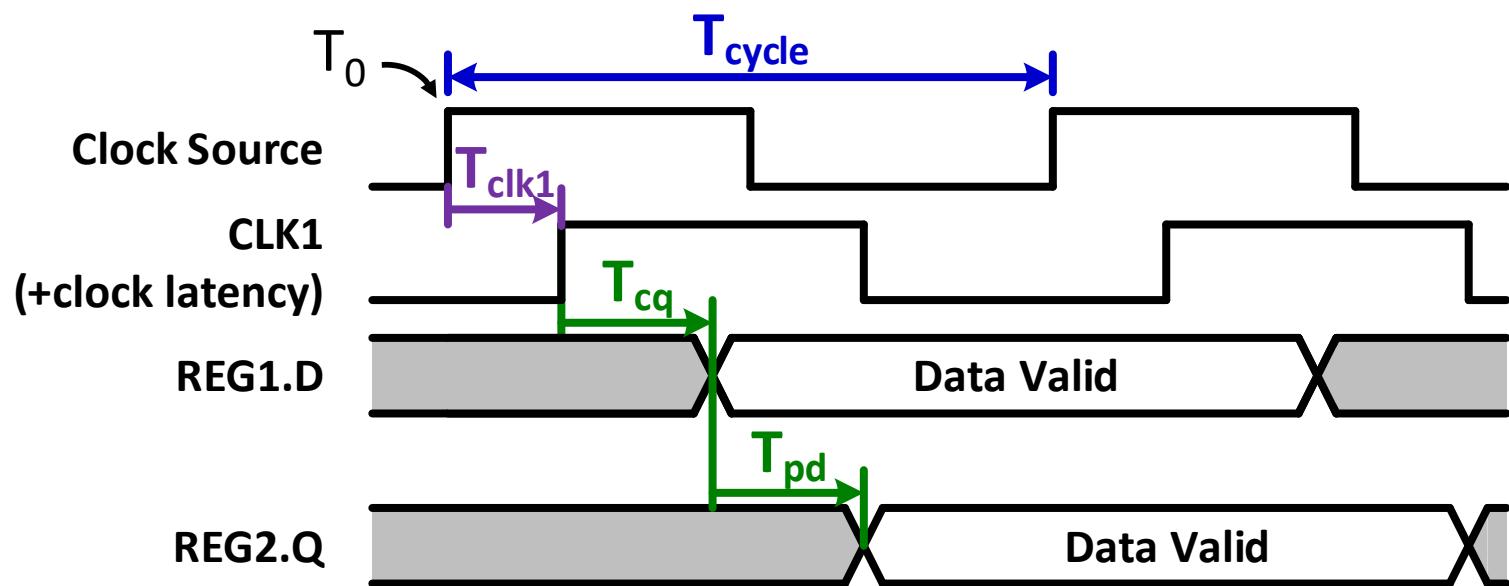

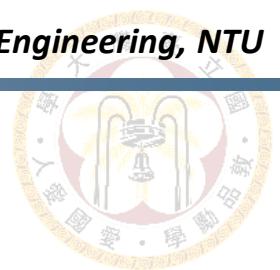
$$\text{Arrival time (AT)}: T_0 + T_{clk1} + T_{cq} + T_{pd}$$




Setup Check: Required Time

- Consider the same circuits in p. 19

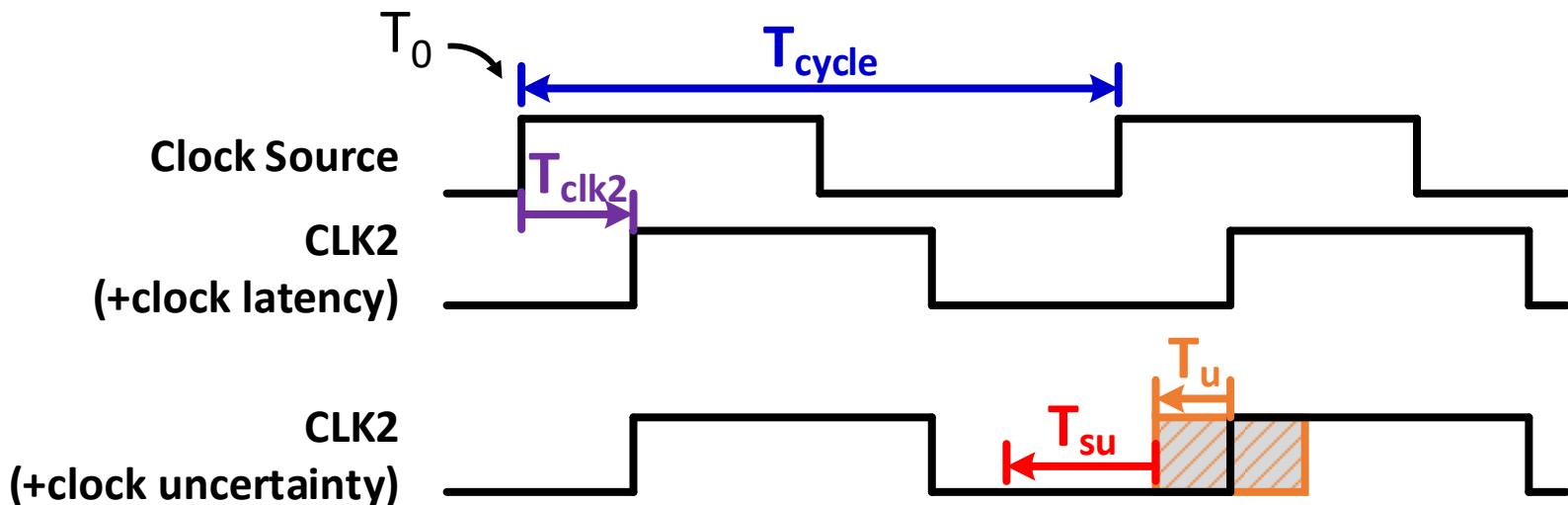


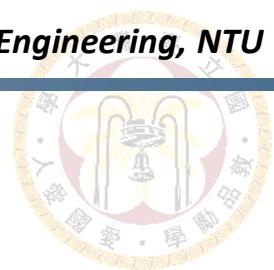Required time (RT): $T_0 + T_{clk2} + T_{cycle} - T_u - T_{su}$




Hold Check: Arrival Time

- Consider the same circuits in p. 20

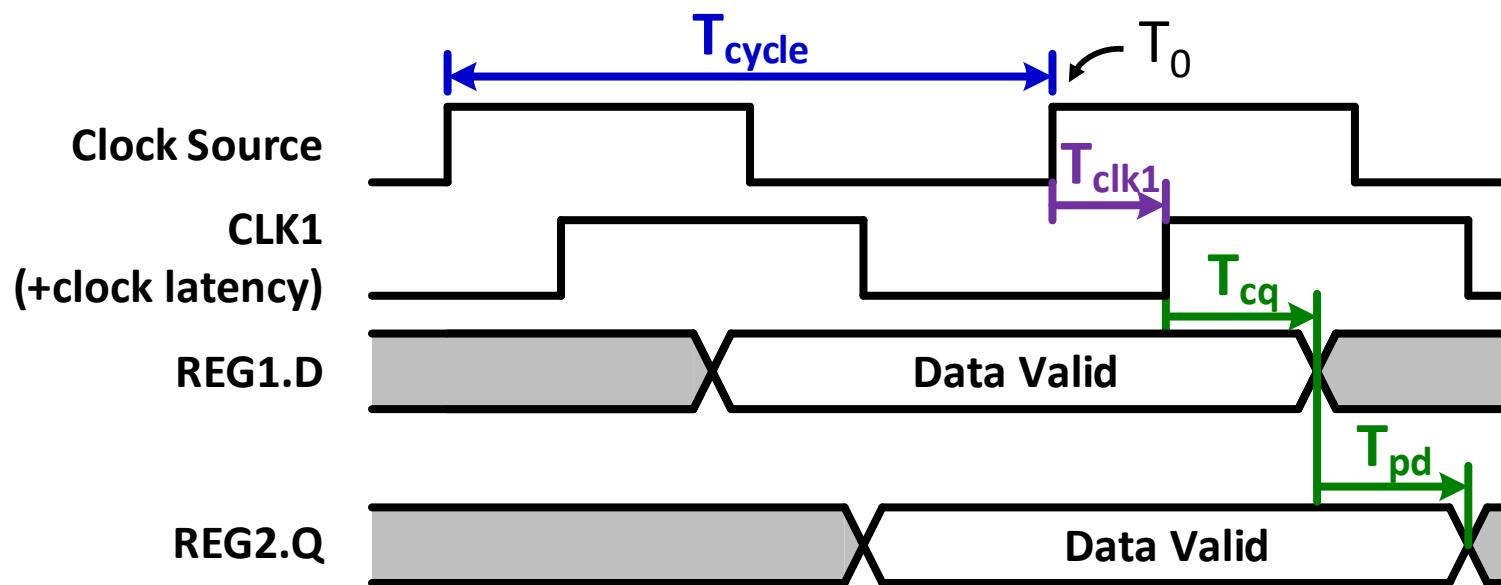

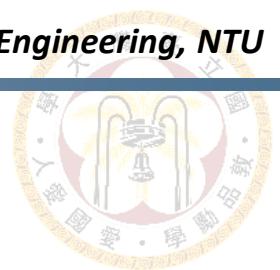
$$\text{Arrival time (AT)}: T_0 + T_{clk1} + T_{cq} + T_{pd}$$




Hold Check: Required Time

- Consider the same circuits in p. 20

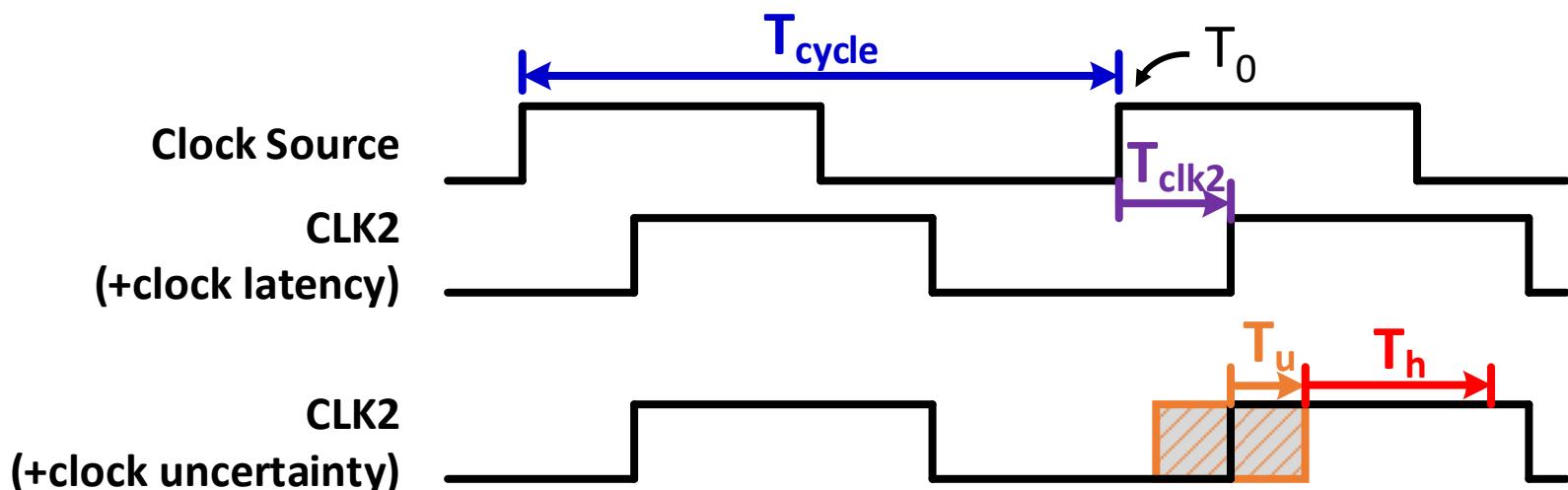


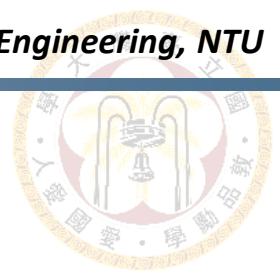
Required time (RT): $T_0 + T_{clk2} + T_u + T_h$



Steps of STA

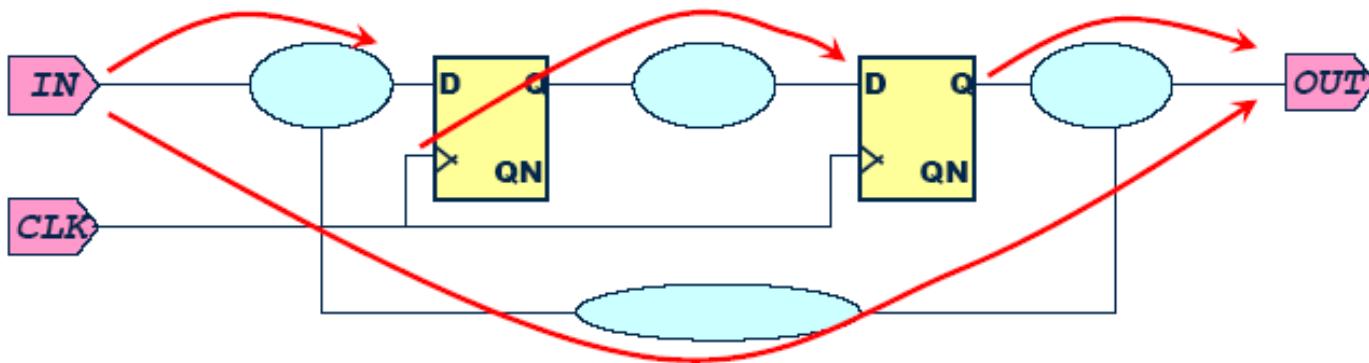1. Break the design into a set of timing paths
2. Calculate arrival time and required time of each path
3. Calculate the slack of each path



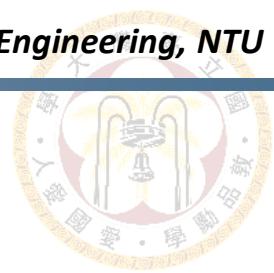

Slack


- **Setup: data should arrive before required time**

$$\text{Setup slack} = \text{RT} - \text{AT}$$

- **Hold: data should be held until required time**

$$\text{Hold slack} = \text{AT} - \text{RT}$$

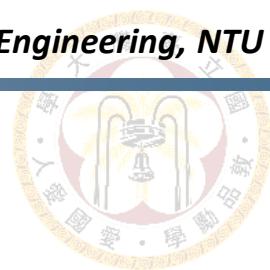- **Slack $\geq 0 \rightarrow$ timing constraints met**
- **Slack $< 0 \rightarrow$ timing constraints violated**



Critical Path

- The path with the worst negative slack (WNS)

Report : timing -path full -delay max		
-max_paths 1		
Design : MUL		


Point	Incr	Path

-		
clock CLK (rise edge)	0.00	0.00
clock network delay (ideal)	0.00	0.00
IN1_R_reg[14]/CK (DFFHQX4)	0.00	0.00 r
IN1_R_reg[14]/Q (DFFHQX4)	0.30	0.30 r
U14/Y (BUFX20)	0.18	0.48 r
mult_21/A[14]		
(MUL_DW02_mult_16_16_0)	0.00	0.48 r
... (ignored)		
mult_21/PRODUCT[28]		
(MUL_DW02_mult_16_16_0)	0.00	4.91 r
OUT_reg[28]/D (DFFXL)	0.00	4.91 r
data arrival time		4.91


clock CLK (rise edge)	4.00	4.00
clock network delay (ideal)	0.00	4.00
OUT_reg[28]/CK (DFFXL)	0.00	4.00 r
library setup time	-0.10	3.90
data required time		3.90

data required time		3.90
data arrival time		-4.91

slack (VIOLATED)		-1.00

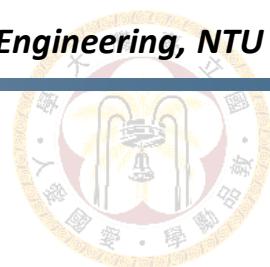


Path-based vs. Block-based STA

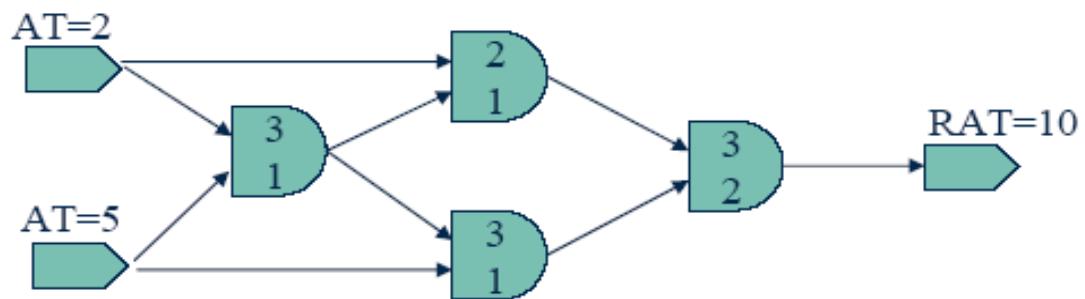


Path-based:

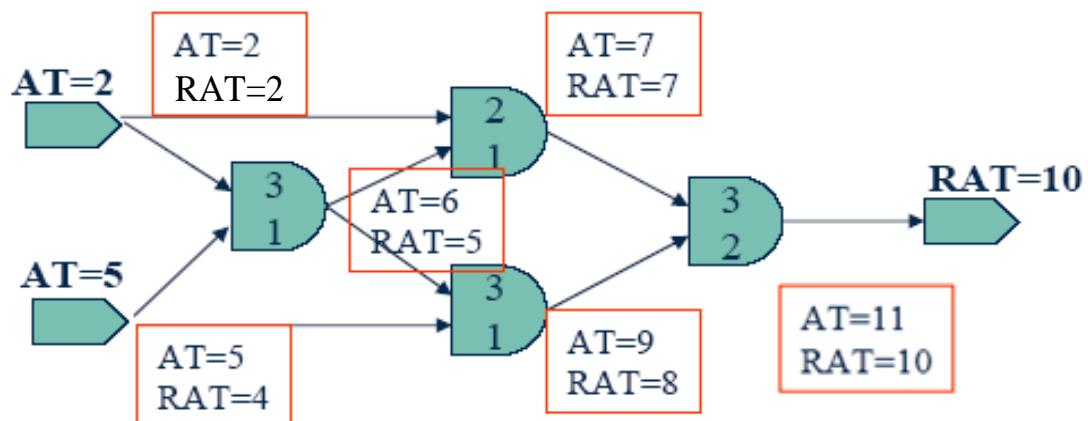- $2+2+3 = 7$ (OK)
- $2+3+1+3 = 9$ (OK)
- $2+3+3+2 = 10$ (OK)
- $5+1+1+3 = 10$ (OK)
- $5+1+3+2 = 11$ (Fail)
- $5+1+2 = 8$ (OK)





Block-based:

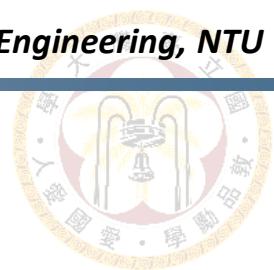Critical path is determined as collection of gates with the same, negative slack:
In our case, we see one critical path with slack = -1





Block-based STA: Arrival Time

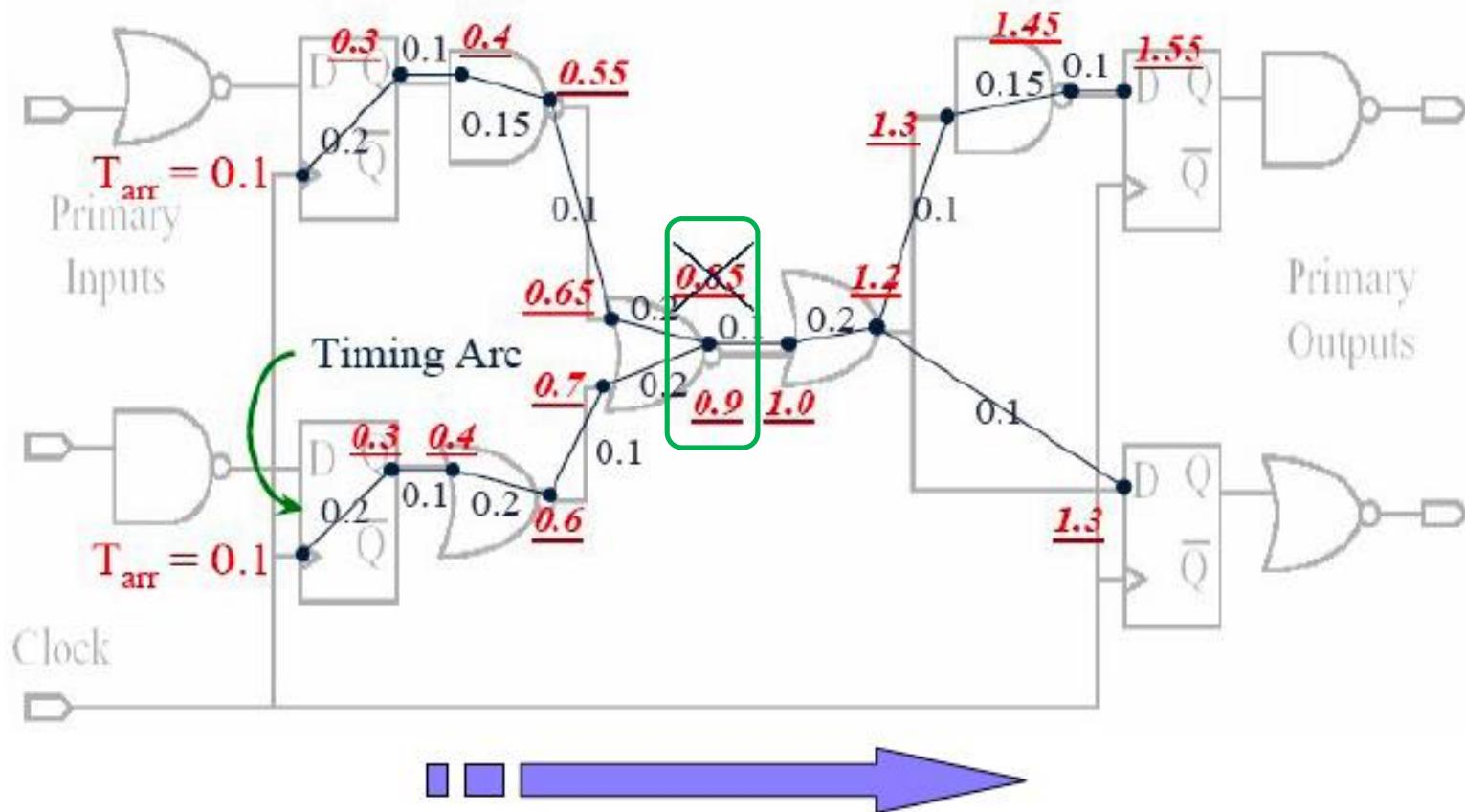

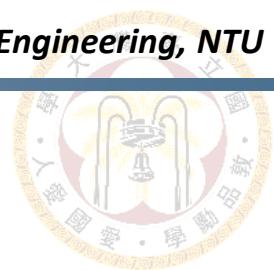


Block-based STA: Required Time

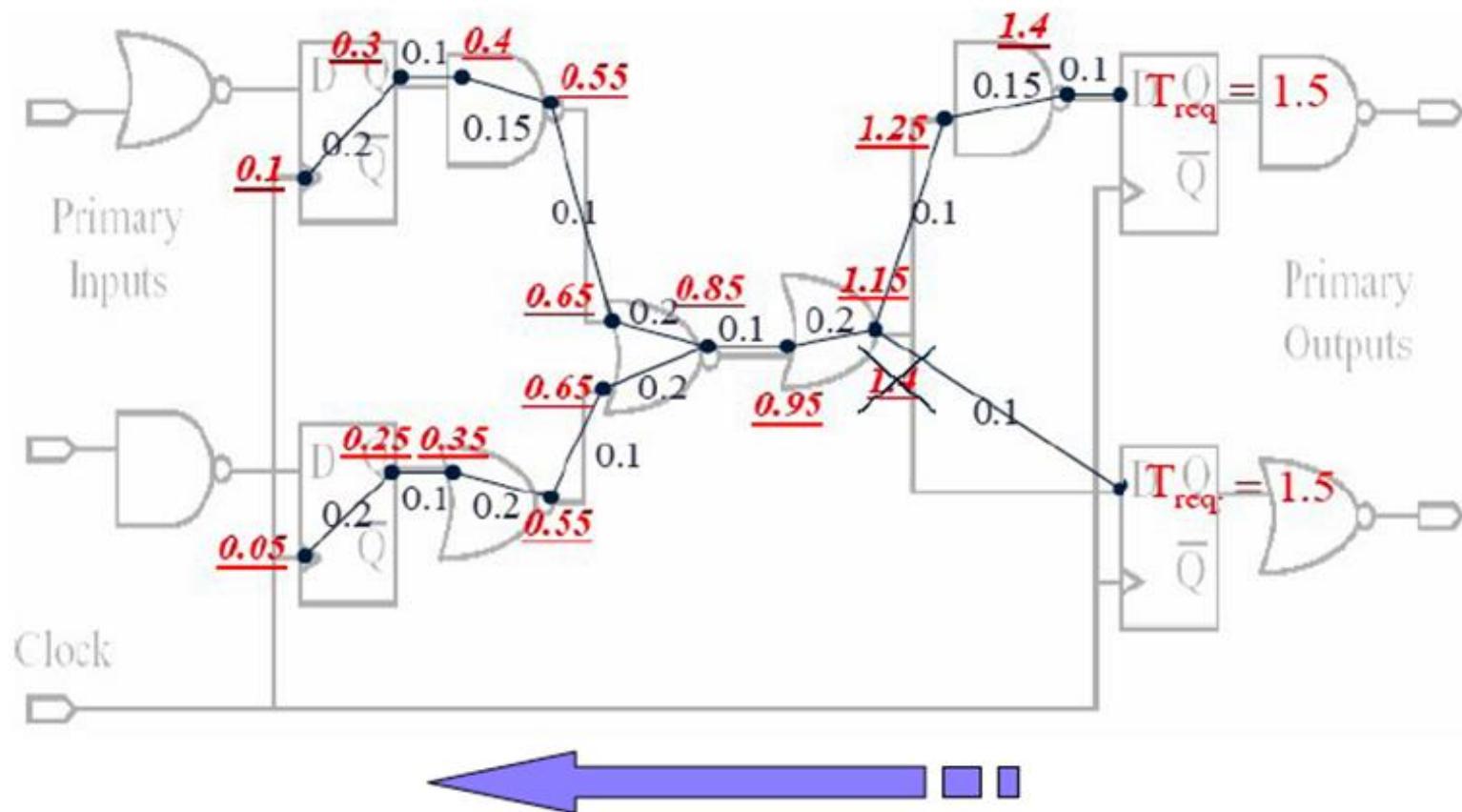

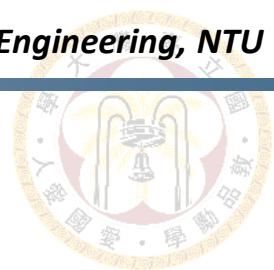


Setup Slack Graph

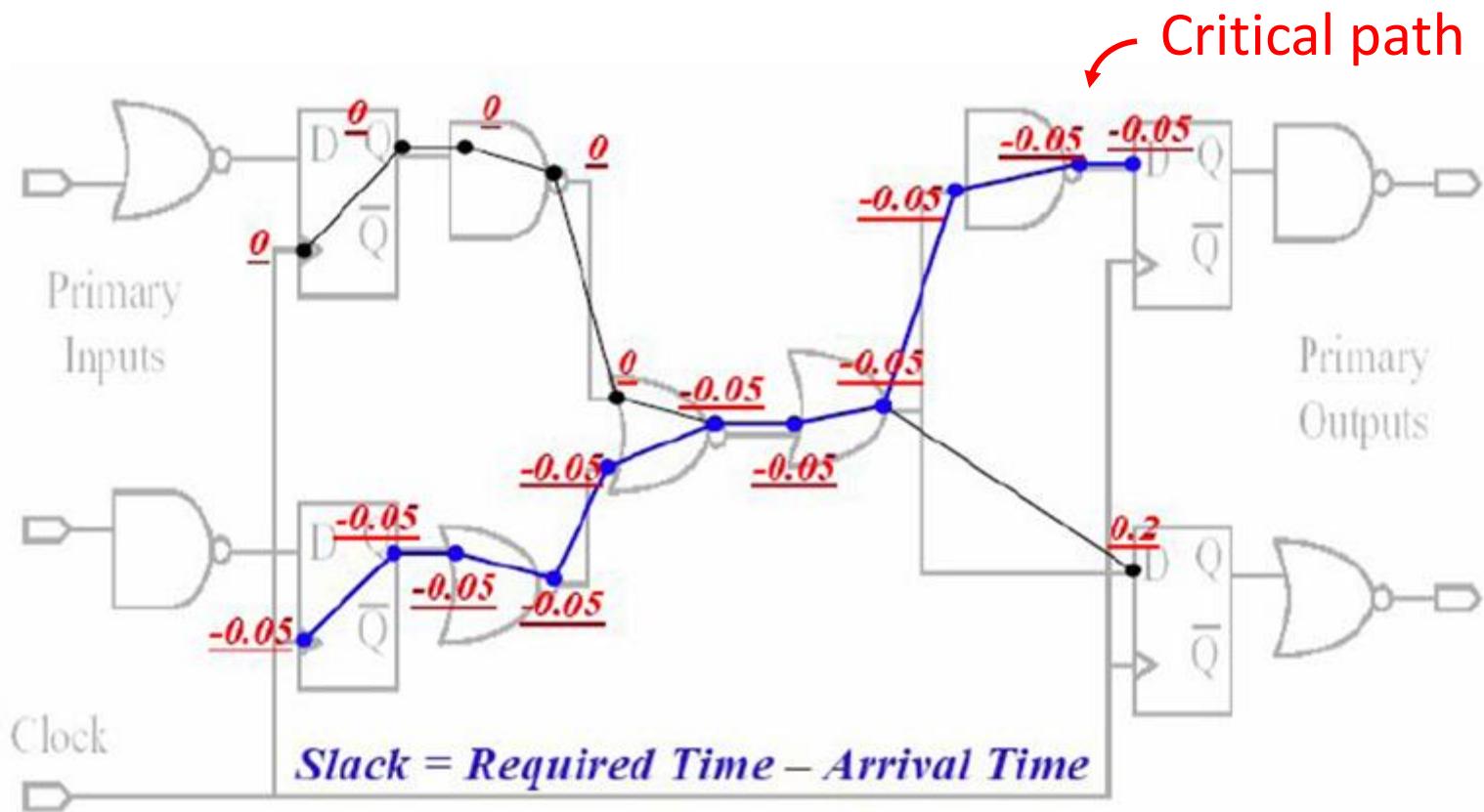


$\text{Slack} \geq 0 \rightarrow \text{timing constraints met}$

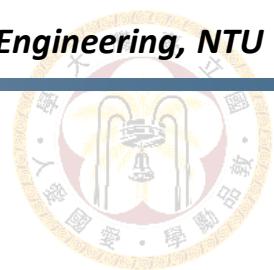$\text{Slack} < 0 \rightarrow \text{timing constraints violated}$




STA Example

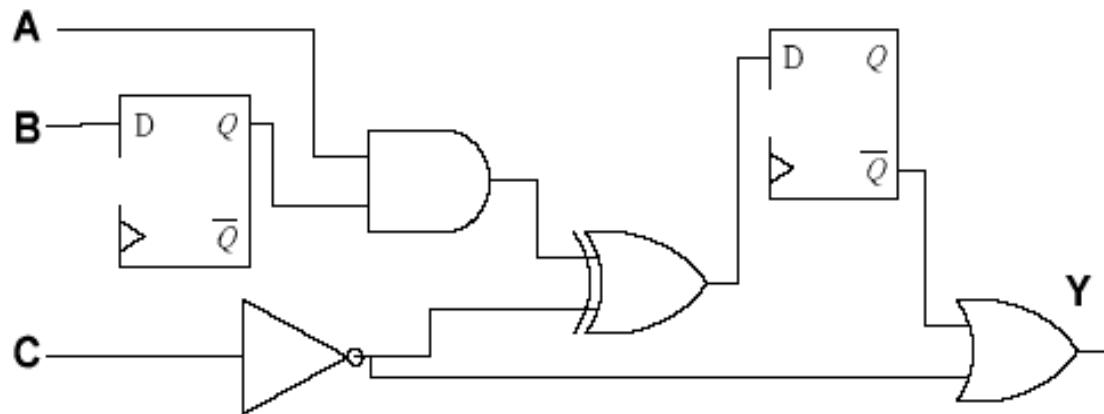

Clock to Q T_{cq}	Setup time T_{su}	Hold time T_h
3ns	1ns	1ns

	Logic gate	Net
Max delay	3ns	2ns
Min delay	1ns	1ns

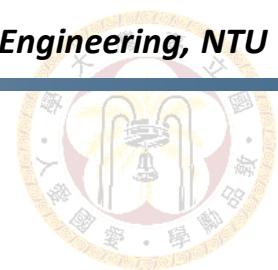


STA Example: Timing Constraints

- Clock definition

Clock period T_{cycle}	Source latency T_{clks}	Network latency T_{clk_n}	Uncertainty T_u
14ns	2ns	3ns	1ns


- IO constraints


	D_A	D_B	D_C	D_Y
Delay	1ns	1ns	1ns	3ns

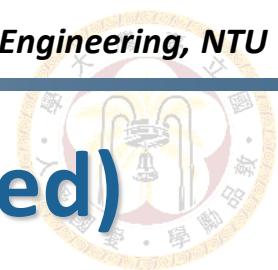


STA Example: Setup Check (Path-based)

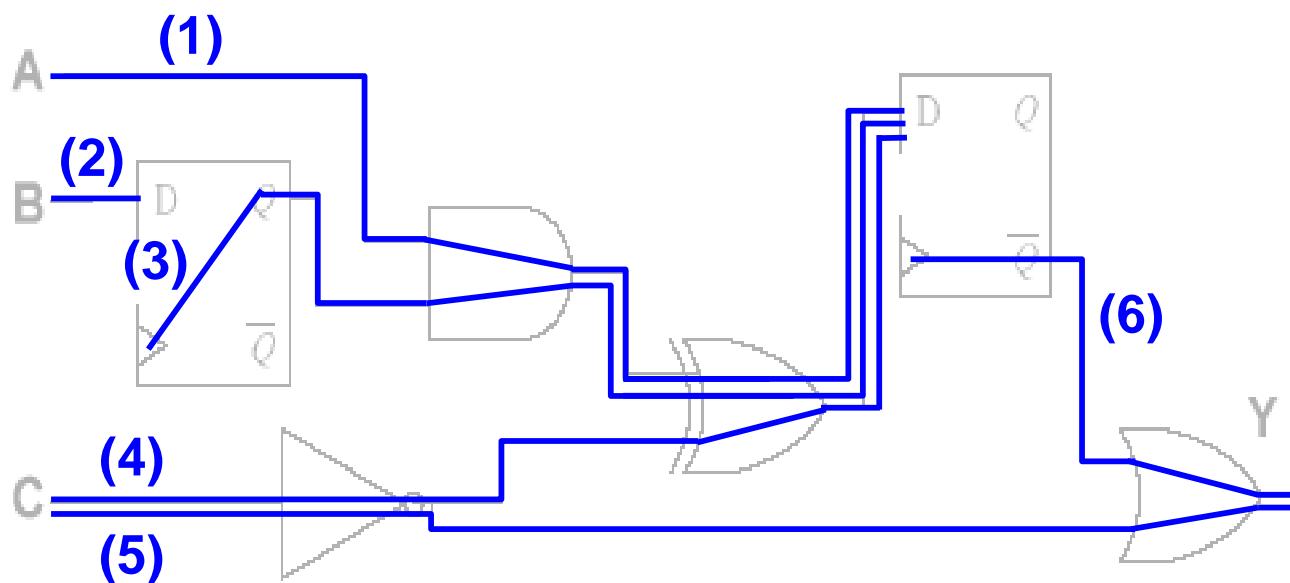- Find out all the timing paths in this design and calculate the slack of each path
 - 6 timing paths in this design



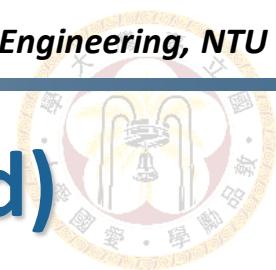

STA Example: Setup AT (Path-based)

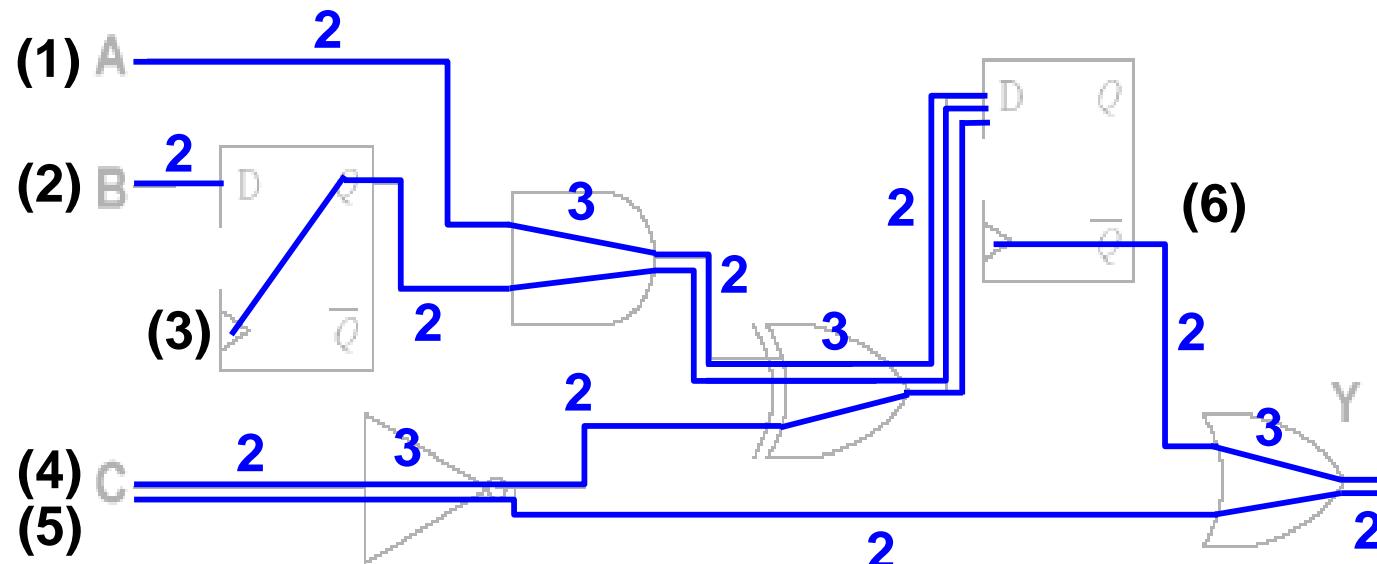

$$(1) D_A + (2+3+2+3+2) = 13$$


$$(4) D_C + (2+3+2+3+2) = 13$$

$$(2) D_B + (2) = 3$$

$$(5) D_C + (2+3+2+3+2) = 13$$


$$(3) T_{\text{clks}} + T_{\text{clk}} + T_{\text{cq}} + (2+3+2+3+2) = 20$$
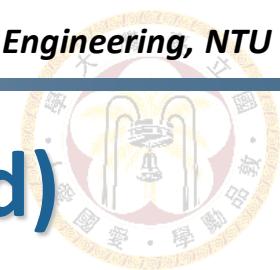
$$(6) T_{\text{clks}} + T_{\text{clk}} + T_{\text{cq}} + (2+3+2) = 15$$




STA Example: Setup RT (Path-based)


- **Timing path (1): input-to-register**
 - RT: $T_{cycle} + T_{clks} + T_{clk_n} - T_u - T_{su} = 14 + 2 + 3 - 1 - 1 = 17\text{ns}$
- **Timing path (2): input-to-register**
 - RT: $T_{cycle} + T_{clks} + T_{clk_n} - T_u - T_{su} = 14 + 2 + 3 - 1 - 1 = 17\text{ns}$
- **Timing path (3): register-to-register**
 - RT: $T_{cycle} + T_{clks} + T_{clk_n} - T_u - T_{su} = 14 + 2 + 3 - 1 - 1 = 17\text{ns}$
- **Timing path (4): input-to-register**
 - RT: $T_{cycle} + T_{clks} + T_{clk_n} - T_u - T_{su} = 14 + 2 + 3 - 1 - 1 = 17\text{ns}$

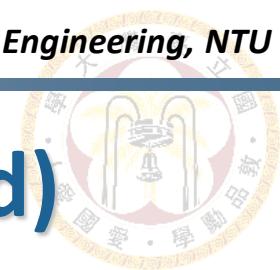


STA Example: Setup RT (Path-based)

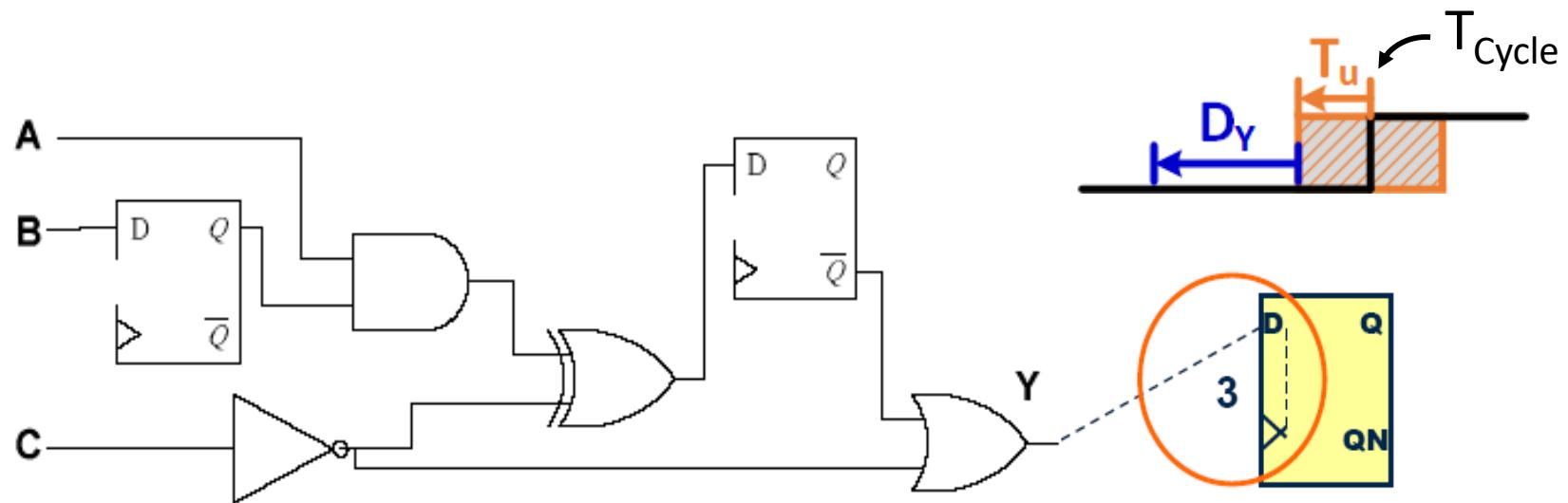- **Timing path (5): input-to-output**
 - RT: $T_{cycle} - T_u - D_Y = 14 - 1 - 3 = 10\text{ns}$
- **Timing path (6): register-to-output**
 - RT: $T_{cycle} - T_u - D_Y = 14 - 1 - 3 = 10\text{ns}$



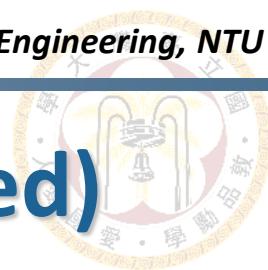

STA Example: Setup Slack (Path-based)

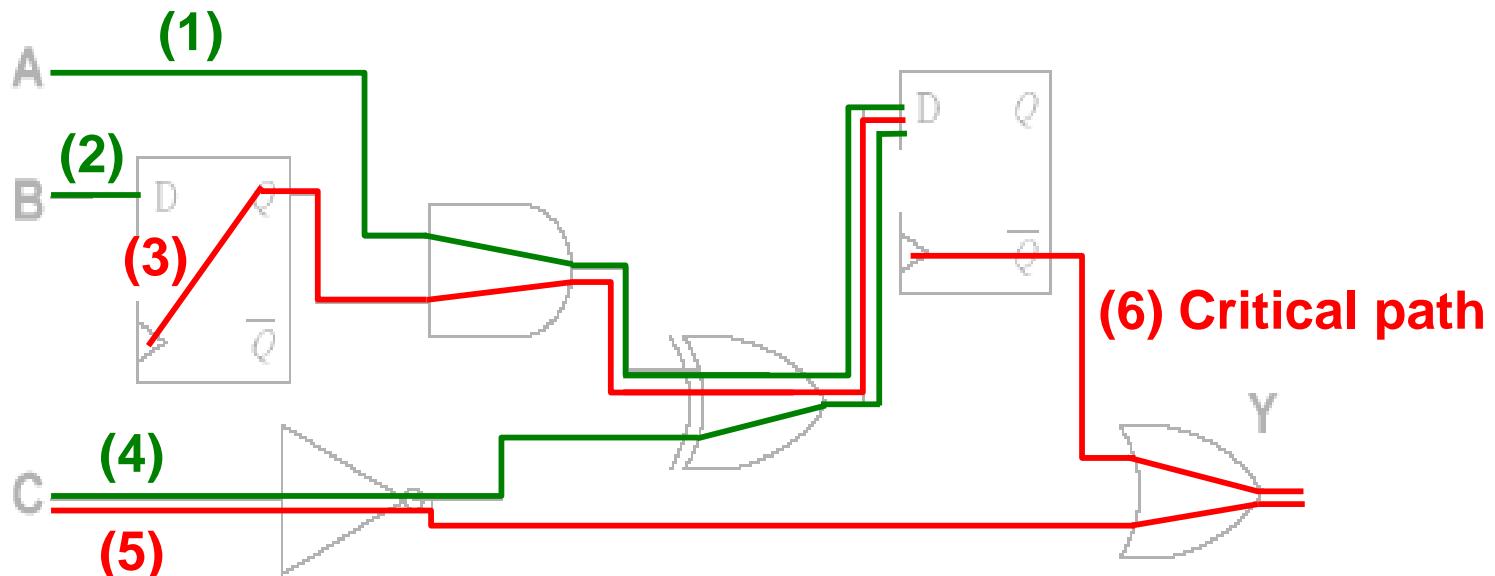

(1) Slack = 17-13 = 4 (met)


(2) Slack = 17-3 = 14 (met)

(3) Slack = 17-20 = -3 (violated)

(4) Slack = 17-13 = 4 (met)


(5) Slack = 10-13 = -3 (violated)


(6) Slack = 10-15 = -5 (violated)

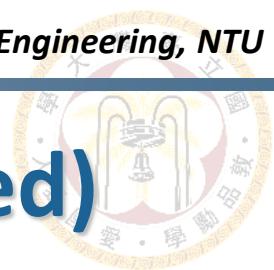


STA Example: Hold Check (Path-based)

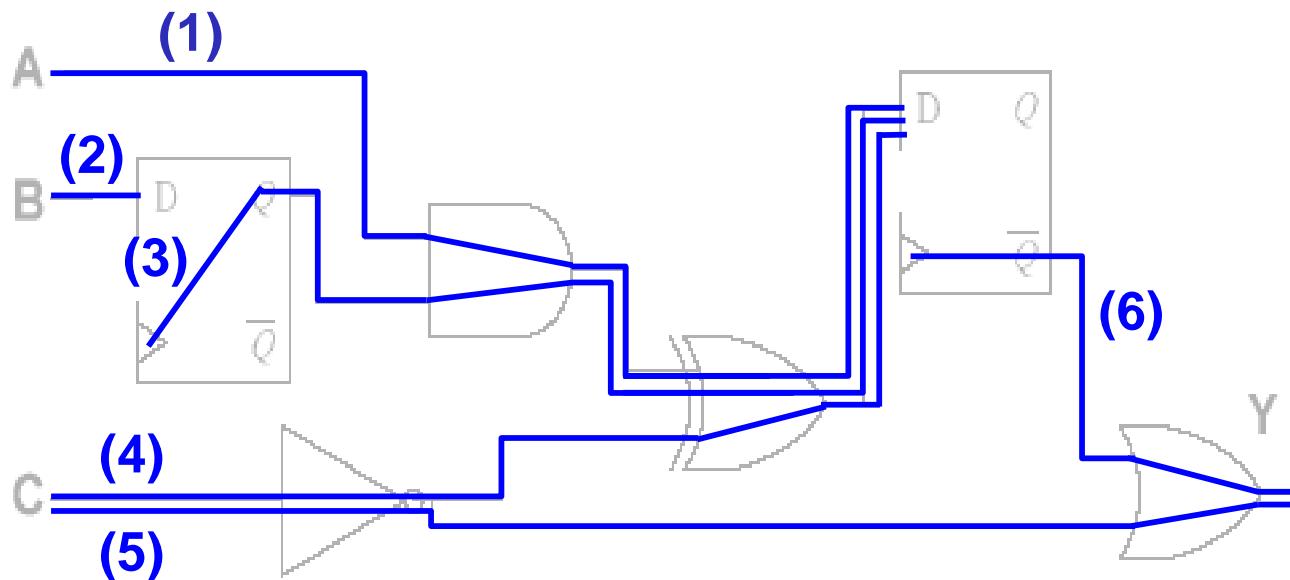- Find out all the timing paths in this design and calculate the slack of each path
 - 6 timing paths in this design



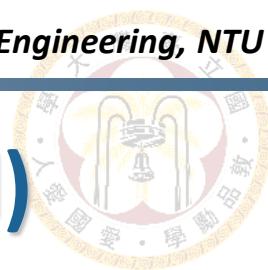

STA Example: Hold AT (Path-based)

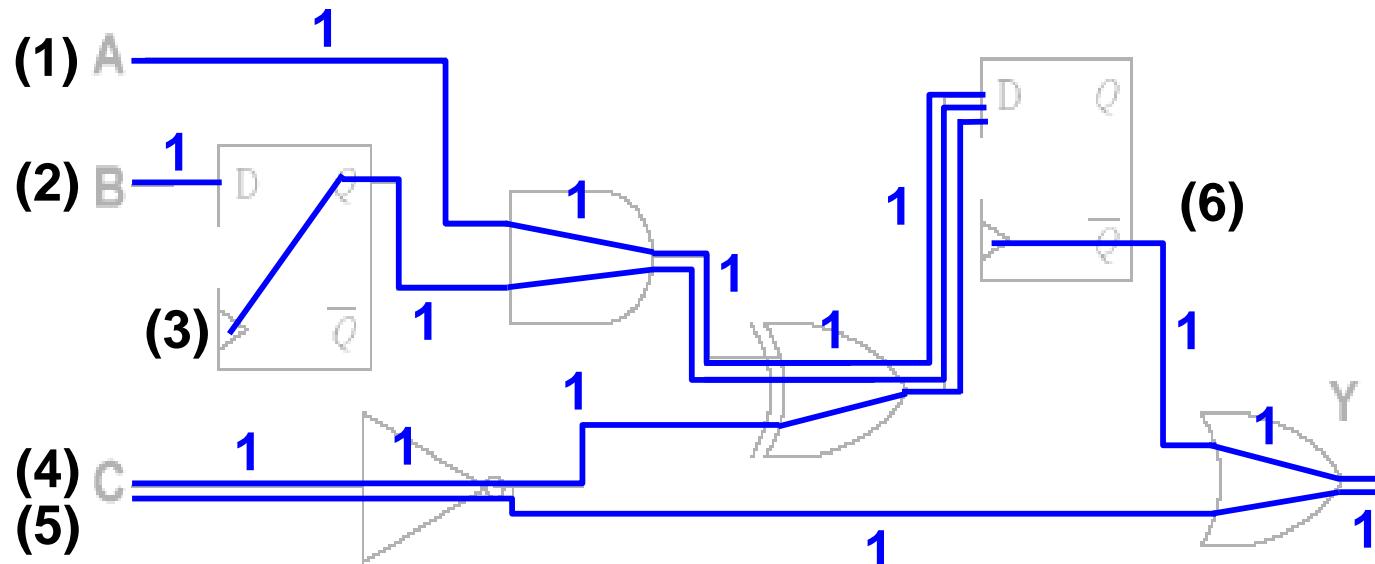

$$(1) D_A + (1+1+1+1+1) = 6$$


$$(4) D_C + (1+1+1+1+1) = 6$$

$$(2) D_B + (1) = 2$$

$$(5) D_C + (1+1+1+1+1) = 6$$


$$(3) T_{\text{clks}} + T_{\text{clk}} + T_{\text{cq}} + (1+1+1+1+1) = 13$$
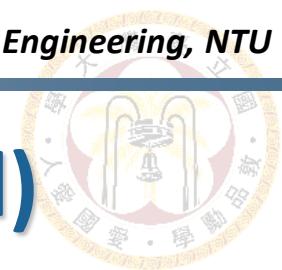
$$(6) T_{\text{clks}} + T_{\text{clk}} + T_{\text{cq}} + (1+1+1) = 11$$




STA Example: Hold RT (Path-based)


- **Timing path (1): input-to-register**
 - RT: $T_{clks} + T_{clk_n} + T_u + T_h = 2 + 3 + 1 + 1 = 7\text{ns}$
- **Timing path (2): input-to-register**
 - RT: $T_{clks} + T_{clk_n} + T_u + T_h = 2 + 3 + 1 + 1 = 7\text{ns}$
- **Timing path (3): register-to-register**
 - RT: $T_{clks} + T_{clk_n} + T_u + T_h = 2 + 3 + 1 + 1 = 7\text{ns}$
- **Timing path (4): input-to-register**
 - RT: $T_{clks} + T_{clk_n} + T_u + T_h = 2 + 3 + 1 + 1 = 7\text{ns}$

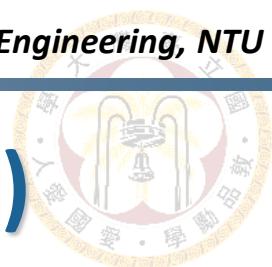


STA Example: Hold RT (Path-based)

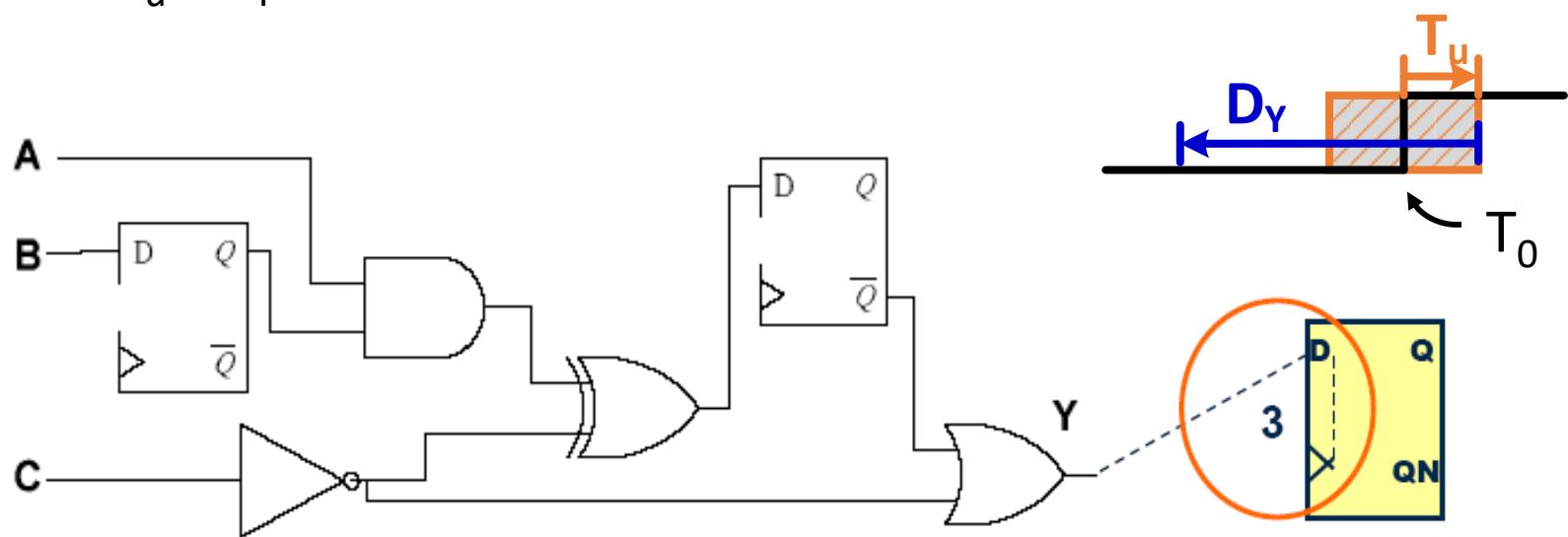- Timing path (5): input-to-output
 - RT: $T_u - D_Y = -2\text{ns}$
- Timing path (6): register-to-output
 - RT: $T_u - D_Y = -2\text{ns}$



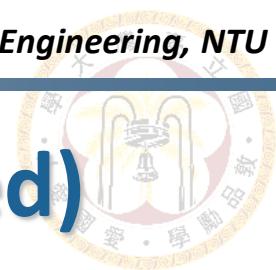

STA Example: Hold Slack (Path-based)

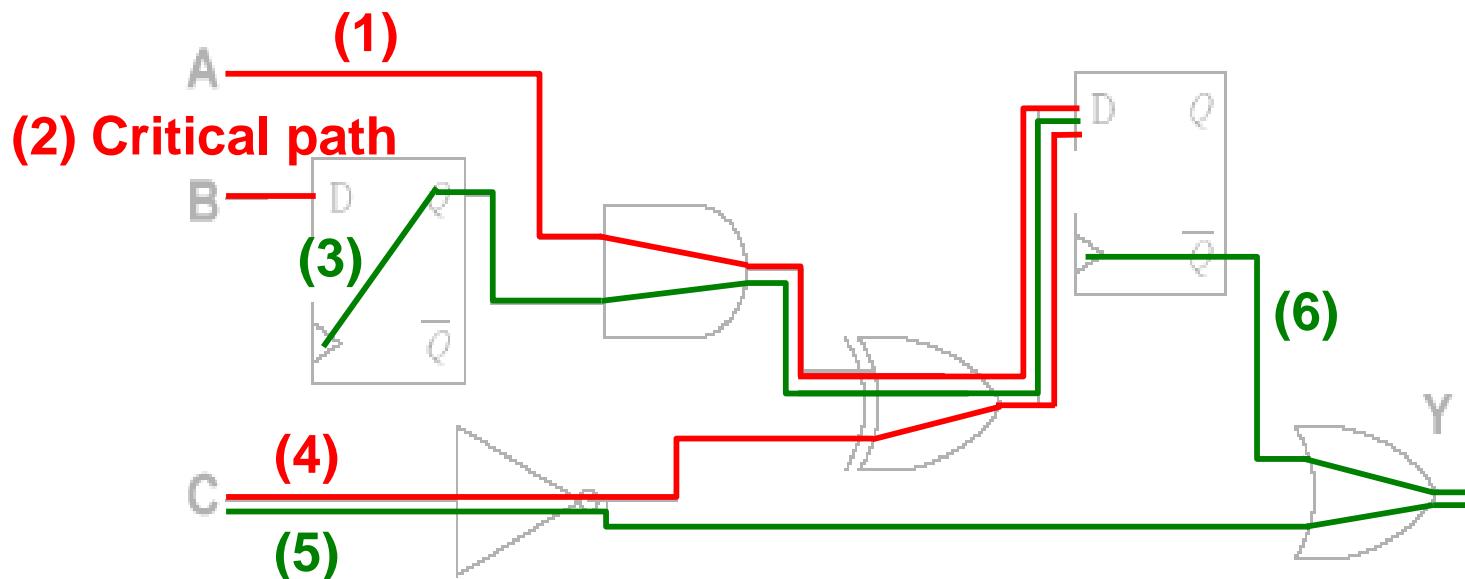

(1) Slack = 6-7 = -1 (**violated**)


(4) Slack = 6-7 = -1 (**violated**)

(2) Slack = 2-7 = -5 (**violated**)

(5) Slack = 6-(-2) = 8 (**met**)


(3) Slack = 13-7 = 6 (**met**)


(6) Slack = 11-(-2) = 13 (**met**)

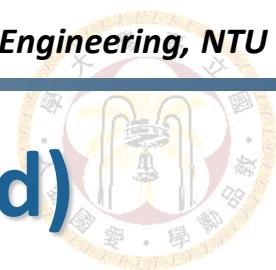

STA Example: Setup AT (Block-based)

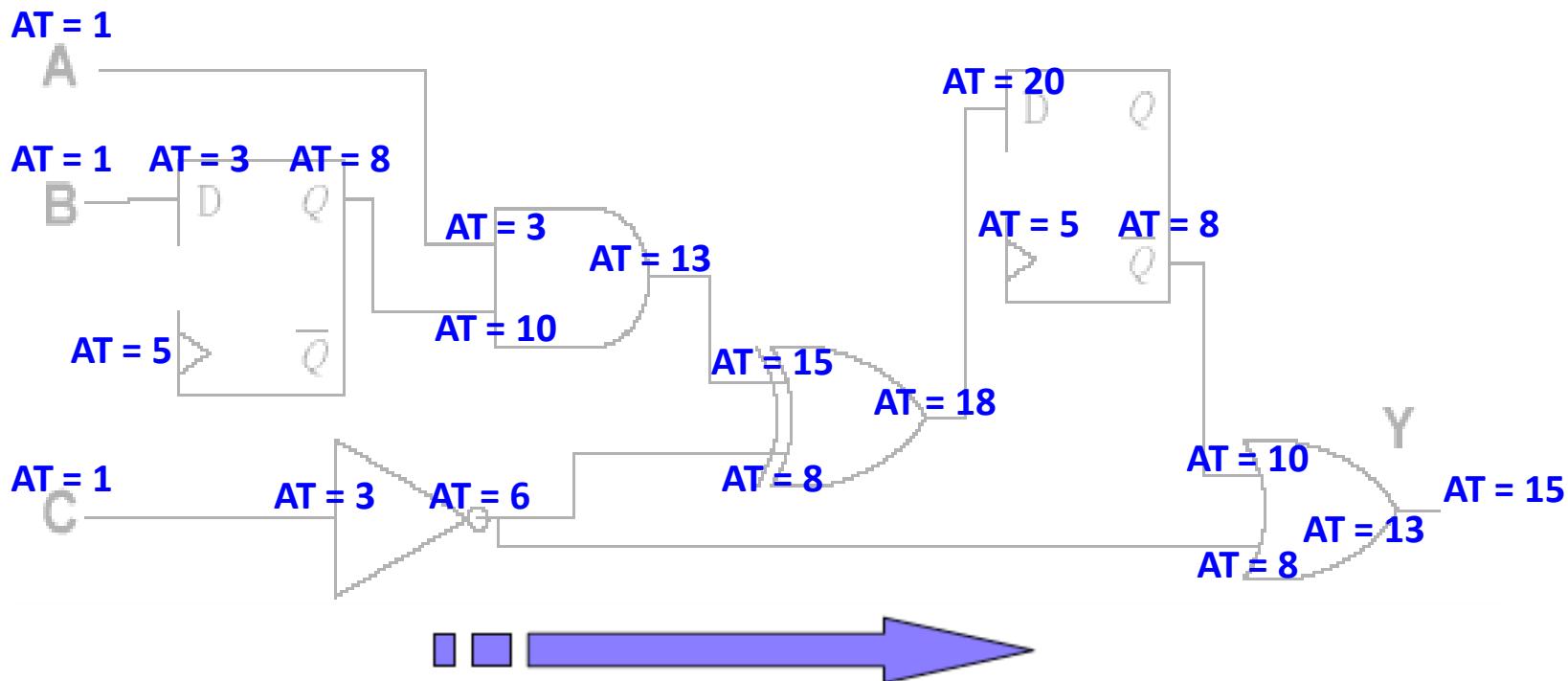
- Calculate the arrival time of each design element
 - Consider **max** AT at the intersection




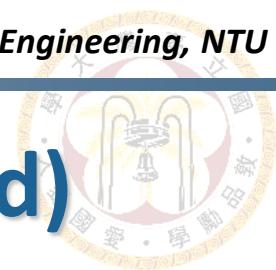

STA Example: Setup RT (Block-based)

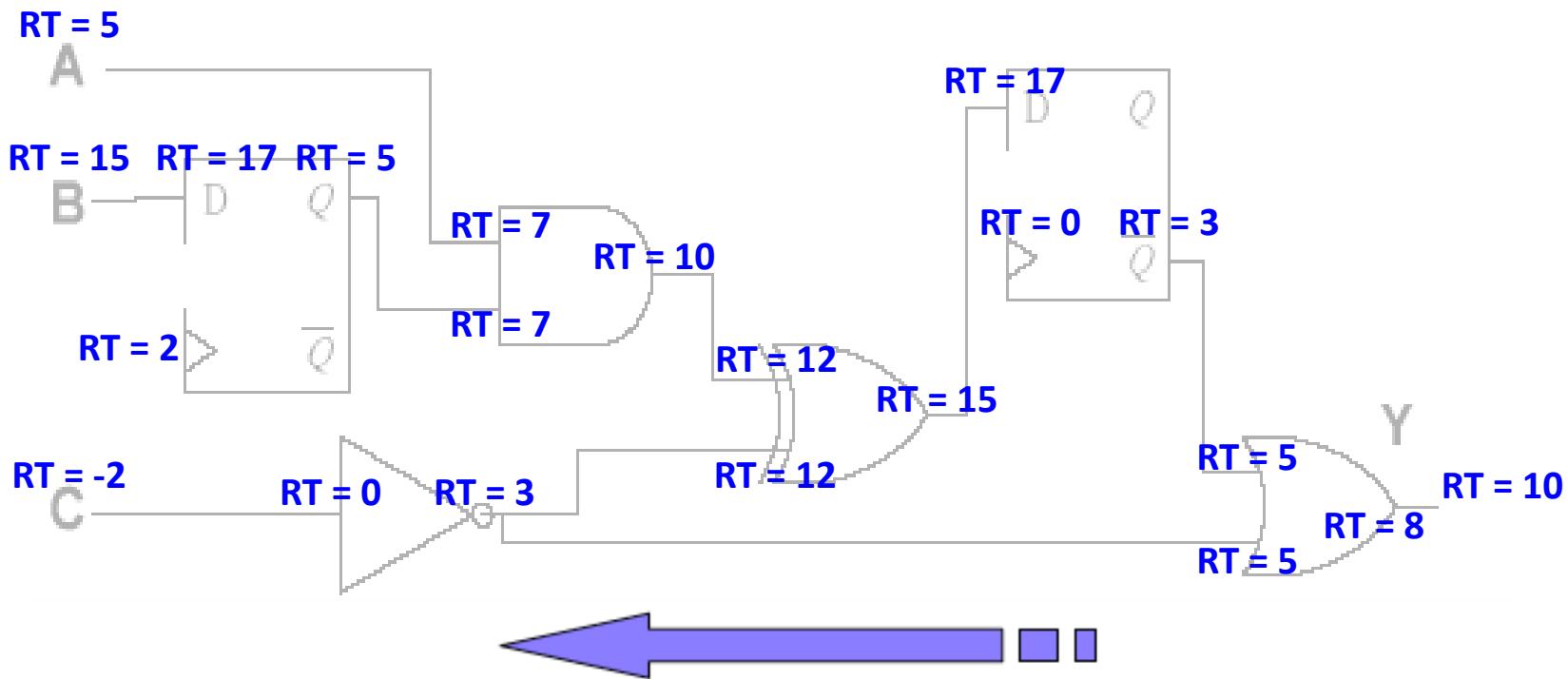
- Calculate the required time of each design element
 - Consider **min** RT at the intersection




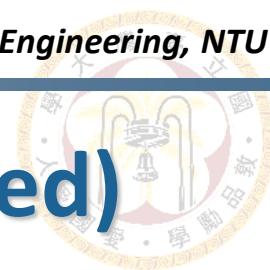

STA Example: Setup Slack (Block-based)

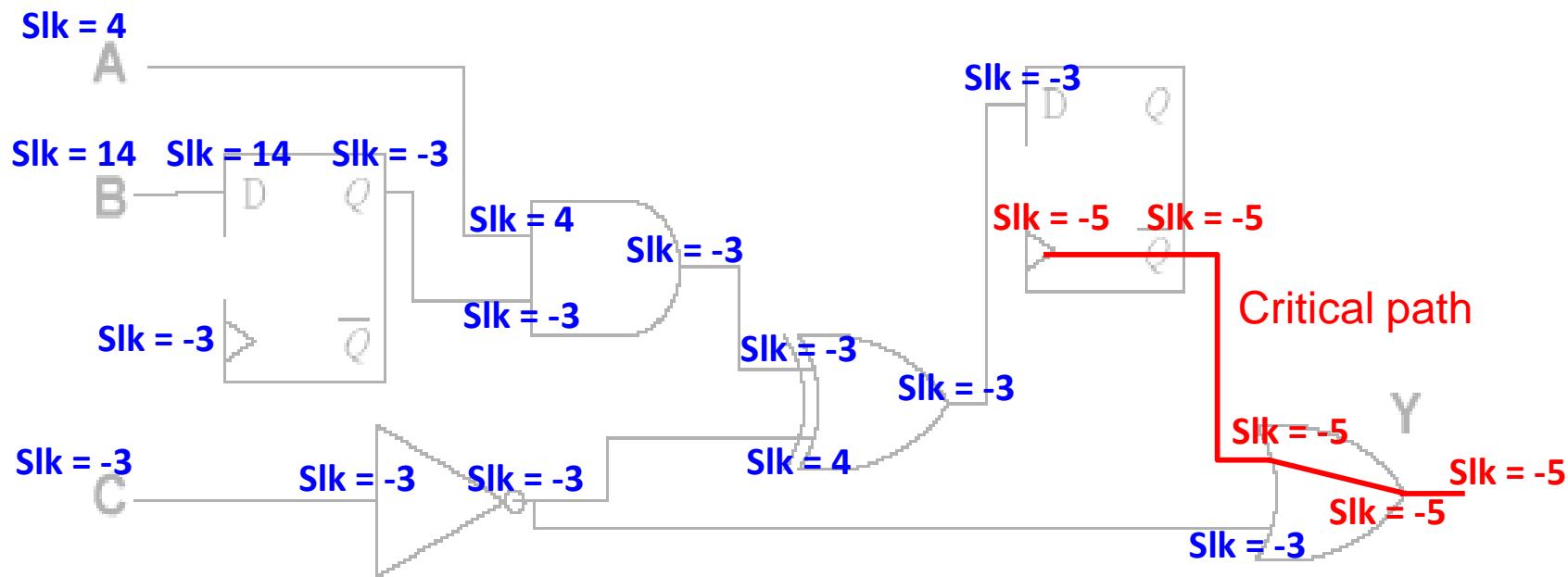
- Calculate the slack (Slk) of each design element
 - $- RT - AT$




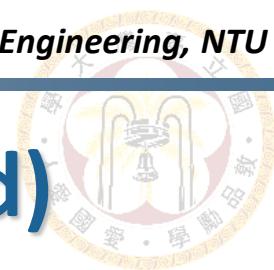

STA Example: Hold AT (Block-based)

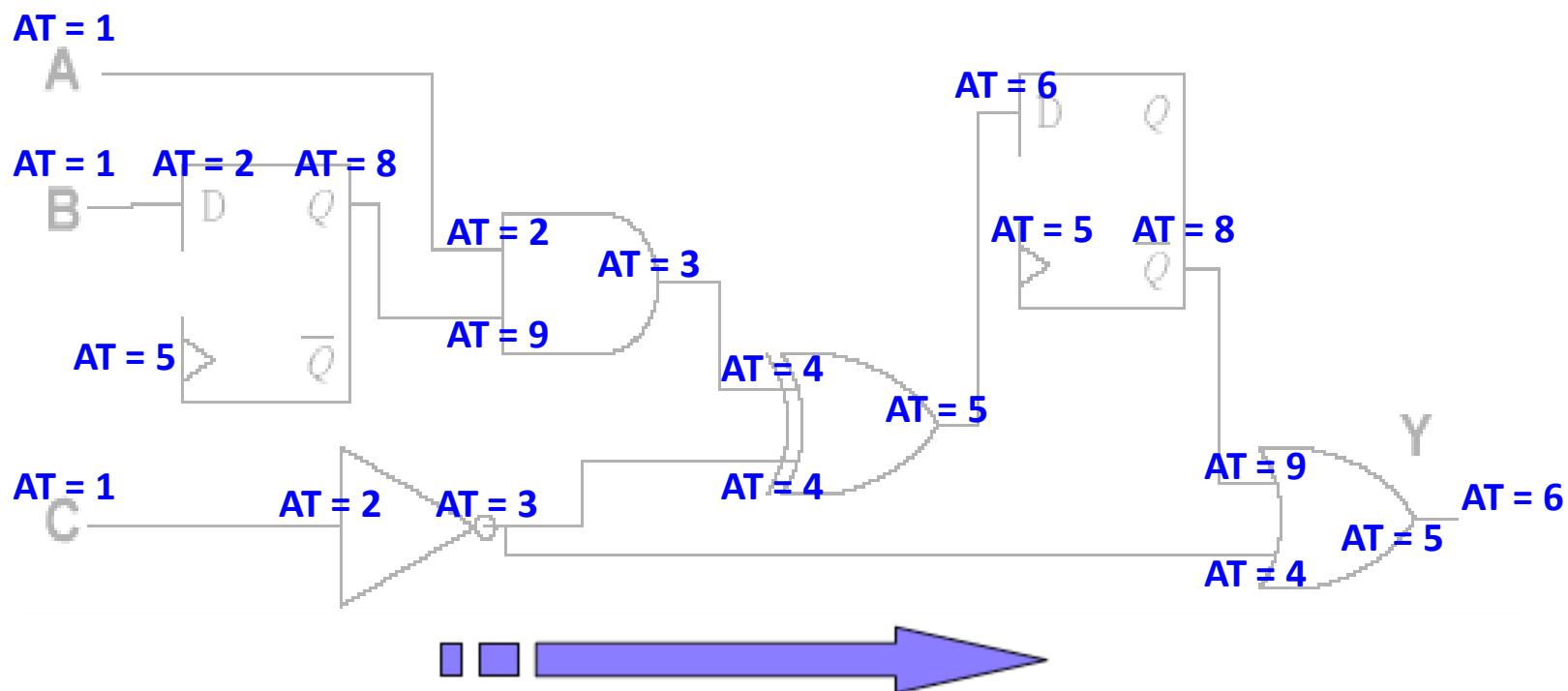
- Calculate the arrival time of each design element
 - Consider **min** AT at each intersection




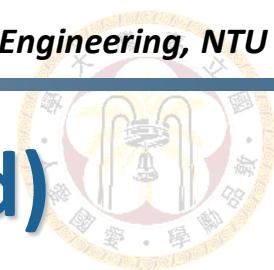

STA Example: Hold RT (Block-based)

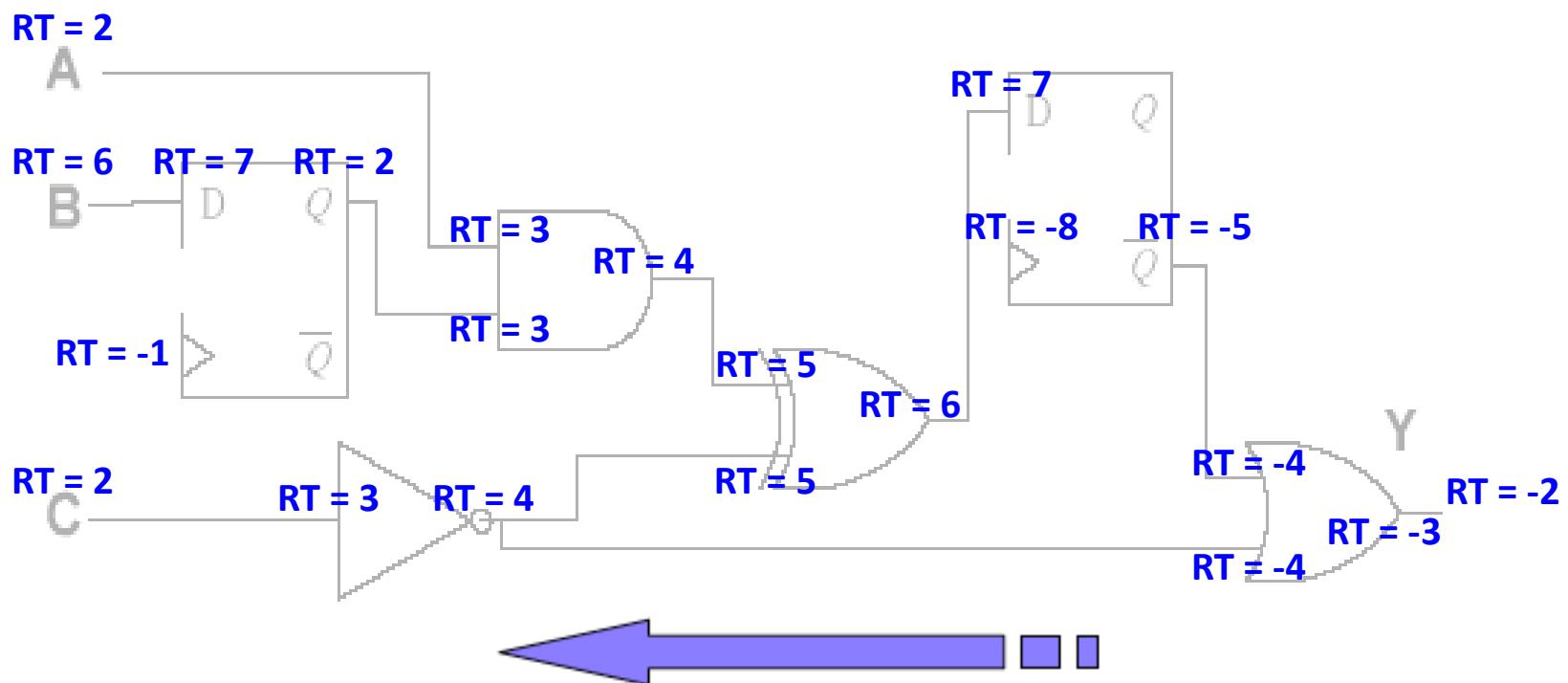
- Calculate the required time of each design element
 - Consider **max** RT at each intersection




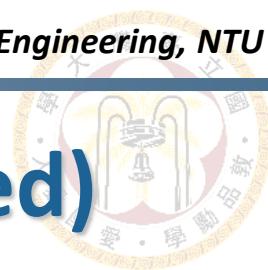

STA Example: Hold Slack (Block-based)

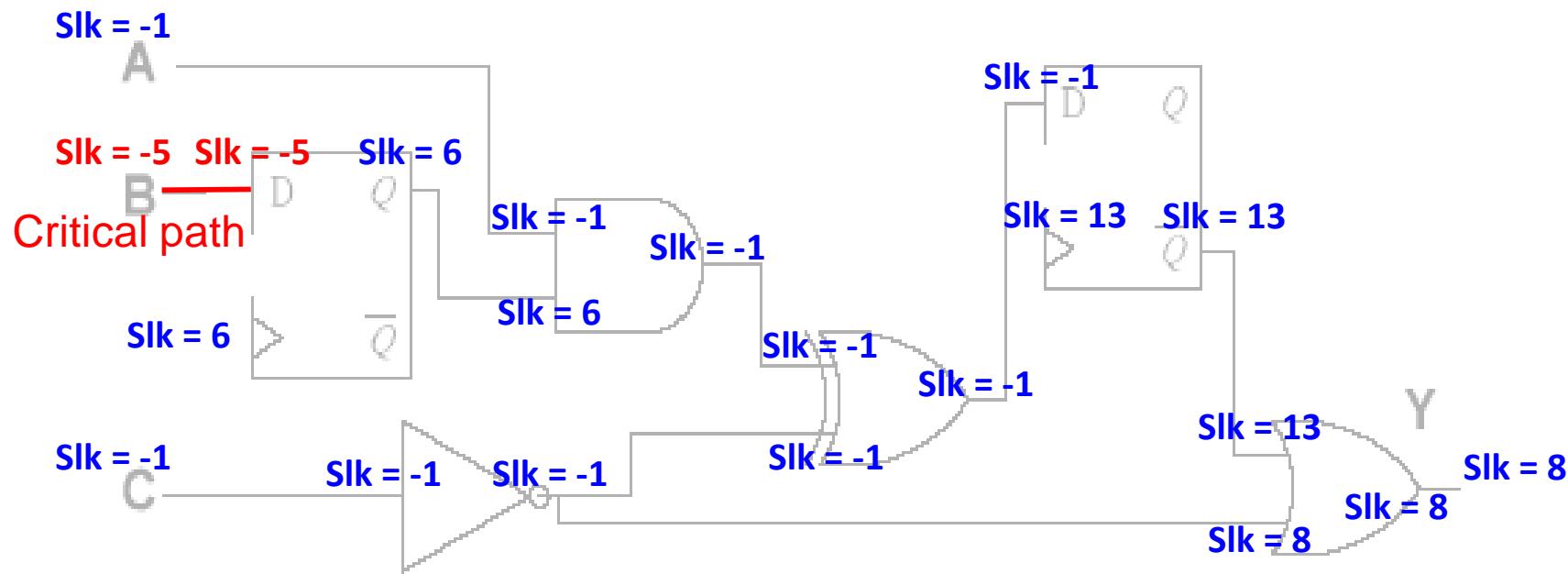
- Calculate the slack (Slk) of each design element
 - $- AT - RT$



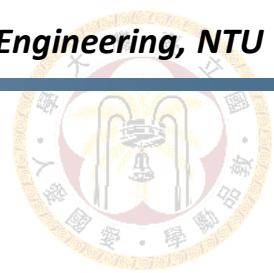


Outline

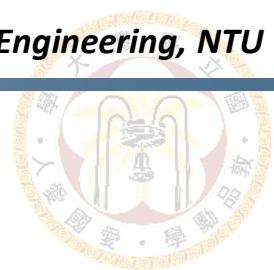- Introduction
- Static Timing Analysis
- **Environment Setting**
- Special Timing Paths




Library Data

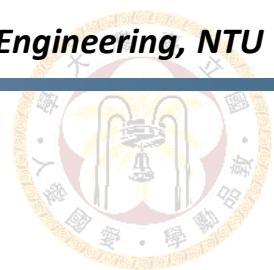- **Cell Delay model**
 - Linear model
 - Non-linear model
- **Operating conditions**
 - set_operating_conditions "typical" -library "typical"
 - set_wire_load_model -name "umc18_wl50" -library "typical"




Linear Cell Delay Model

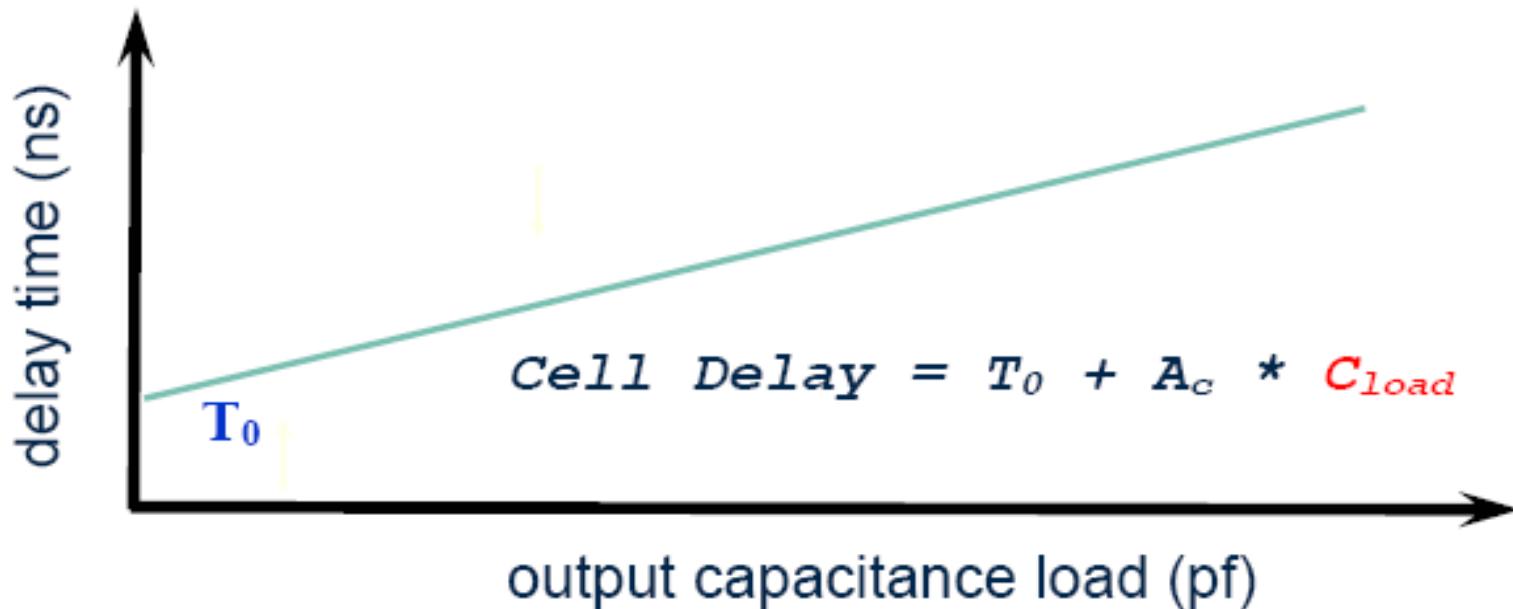



T_0 : cell pin to pin intrinsic delay
(delay without any loading)


A_c : drive impedance

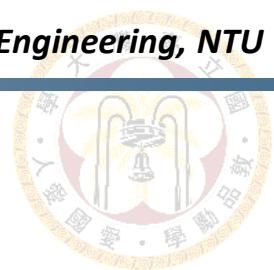

Non-linear Cell Delay Model

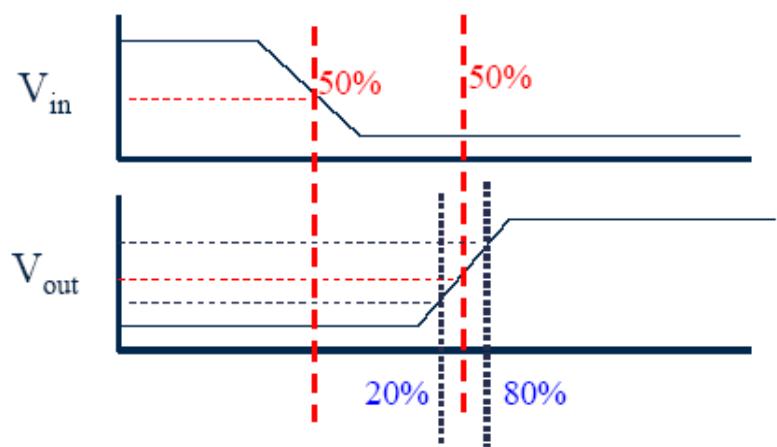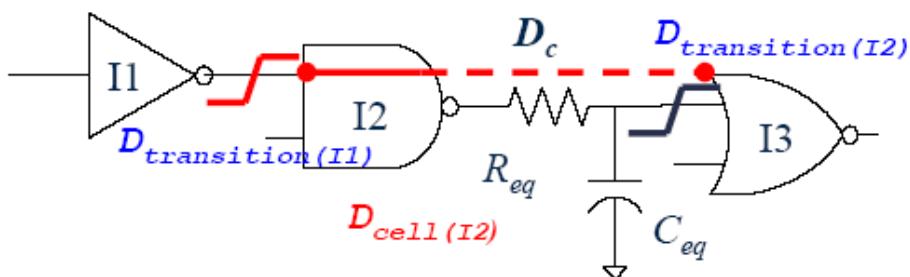- Delay values are stored in the delay tables
 - Cell delay
 - Transition delay
- Interpolation is used



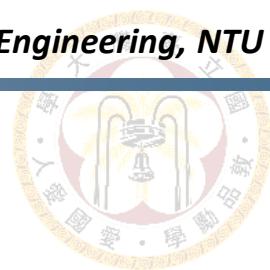

Delay Table

Cell Delay

$$D_{cell(I2)} = f(D_{transition(I1)}, C_{eq})$$


Transition Delay


$$D_{transistion(I2)} = g(D_{transition(I1)}, C_{eq})$$

Output Capacitance	Input Transition		
	0	0.5	1
0.1	0.123	0.234	0.456
0.2	0.222	0.432	0.801

index1: input transition

Index2: output capacitance

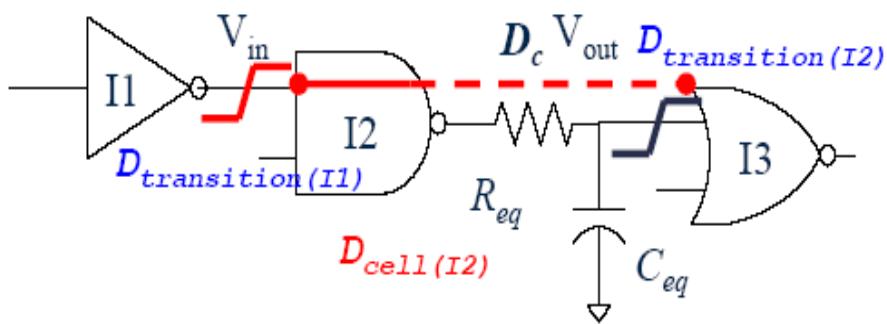

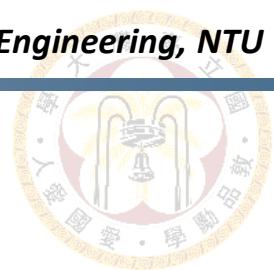




Operating Conditions


- The process, voltage, and temperature (PVT) variation
- Specified in the technology library
- Cell and interconnect delays are scaled

$$D_{scale} = D(1 + \Delta_p K_p)(1 + \Delta_v K_v)(1 + \Delta_t K_t)$$

$\Delta_p = \text{Process - nom_process} / \Delta_v = \text{Voltage - nom_voltage}$

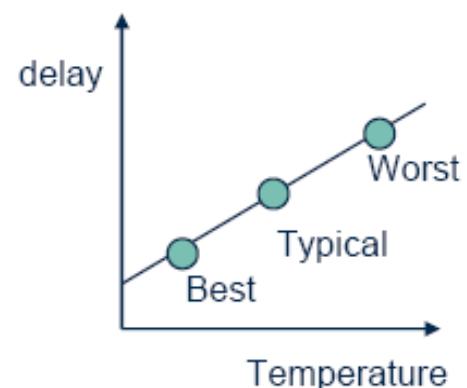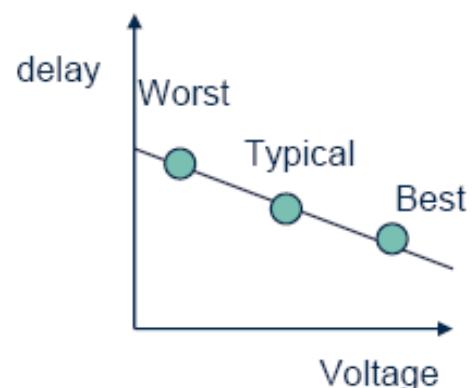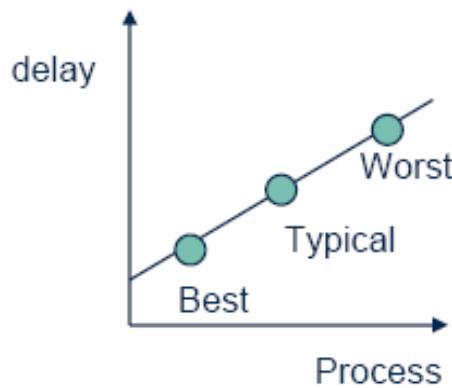
$\Delta_t = \text{Temperature - nom_temperature}$



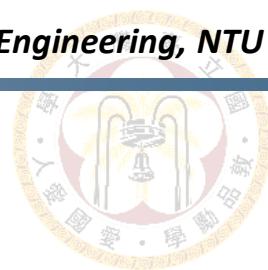


Wireload Model

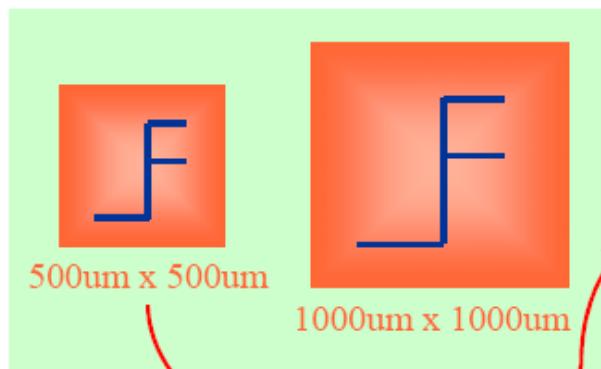- Very inaccurate! (The settings are like that in DC)



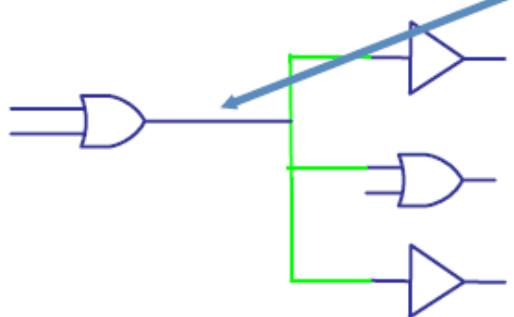
```
wire_load ("500") (  
    resistance : 3.0  
    capacitance: 1.3  
    area: 0.04  
    slop: 0.15  
    fanout_length ( 1 , 2.1 )  
    fanout_length ( 2 , 2.5 )  
    fanout_length ( 3 , 2.8 )  
    fanout_length ( 4 , 3.3 )
```



$$C_{\text{wire}} = (\text{fanout}=3, \text{length }=2.8) \times \text{capacitance coefficient } (1.3) = 3.64 \text{ load units}$$


$$R_{\text{wire}} = (\text{fanout}=3, \text{length }=2.8) \times \text{resistance coefficient } (3.0) = 8.4 \text{ resistance units}$$
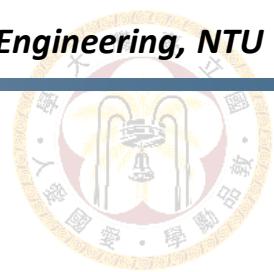
$$\text{Area}_{\text{Net}} = (\text{fanout}=3, \text{length }=2.8) \times \text{area coefficient } (0.04) = 0.112 \text{ net area units}$$




Define Clock Specification

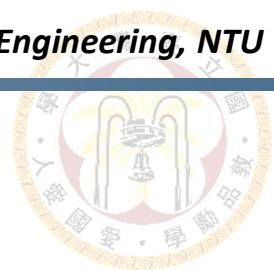
- We need to accurately specify the clock including the clock routing details in the early design stage in order to achieve timing convergence
- What should be defined?
 - Period
 - Waveform
 - Latency
 - Source latency
 - Network latency
 - Uncertainty
- All register-to-register paths are constrained now



Clock Period & Waveform


Period T_{cycle}	Rise time T_{rise}	Fall time T_{fall}
10ns	1ns	1ns

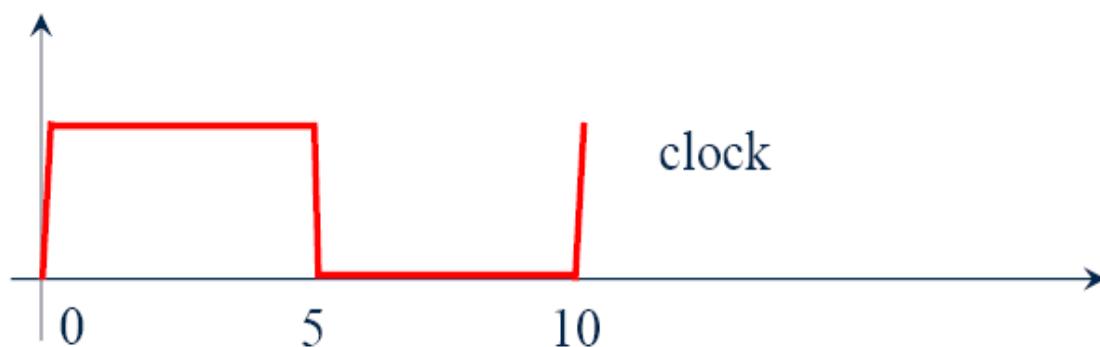

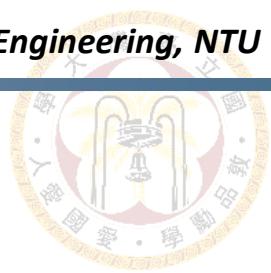


Outline

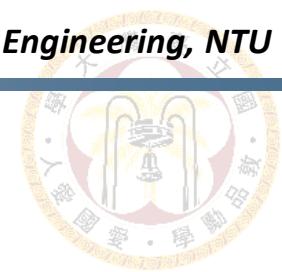- Introduction
- Static Timing Analysis
- Environment Setting
- Special Timing Paths




Special Timing Paths: False Paths

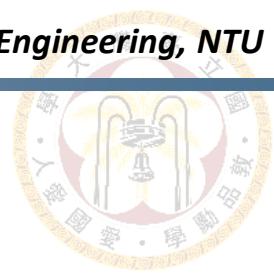
- Timing paths that will be **ignored** during STA
- **5 types of false paths**
 - Unexercised path
 - Irrelevant path
 - Asynchronous path
 - Logically impossible path
 - Combinational loops
- Should be used carefully



Unexercised Path

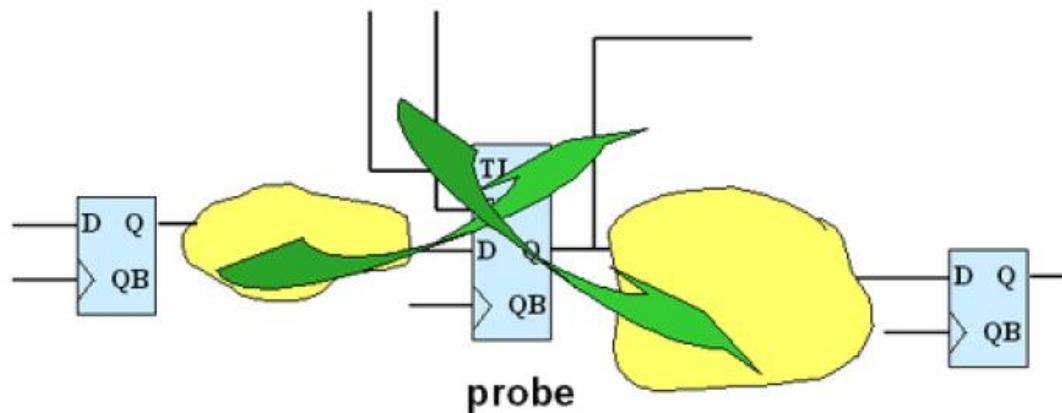
- A path may exist in the circuit but never be used in its normal functional operation
 - A test register “probe” is inserted in the circuit to enable chip debugging in the field
 - Data can be read through the probe register
 - Data can be written from the probe register
 - Probing would not occur at speed




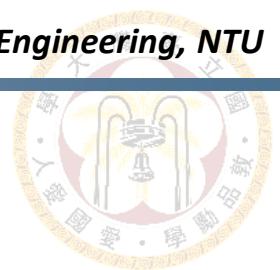

Irrelevant Path

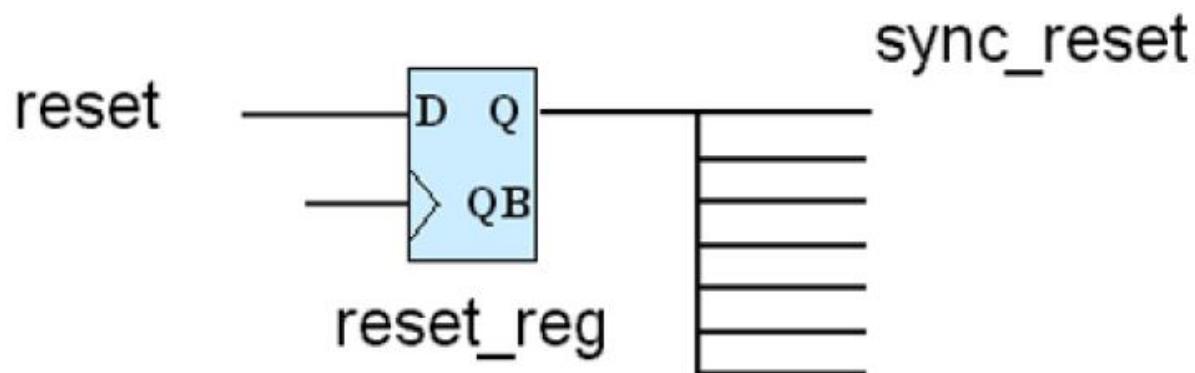
- A functional path which its timing is so slow or irrelevant
 - The chip uses a synchronous reset. The reset cycle has a huge number of cycles before it needs to settle




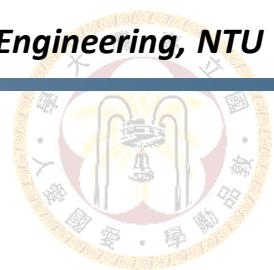

Asynchronous Path

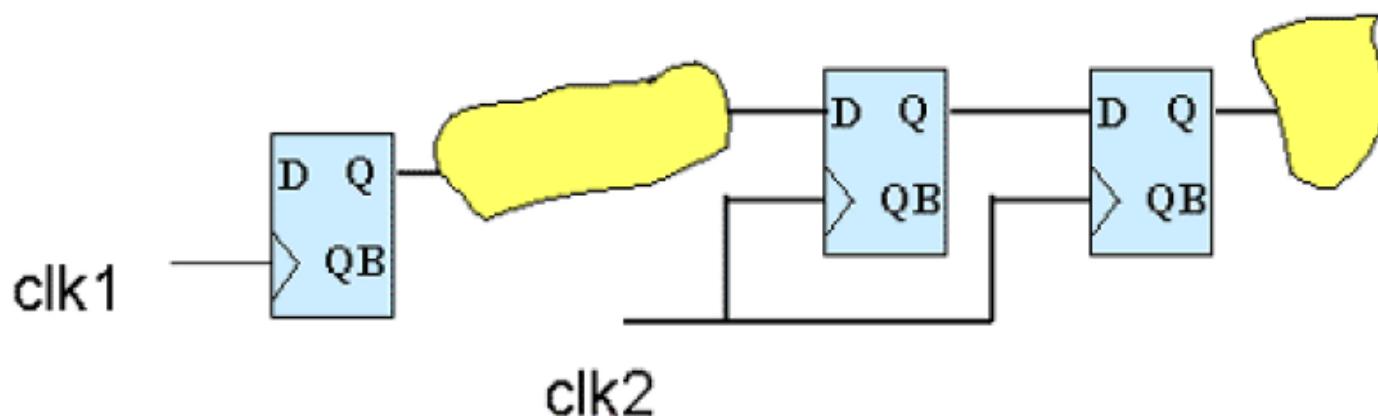
- A path between 2 different clock domains
 - Clock domain crossing (CDC): transfer data from clk 1 to clk 2




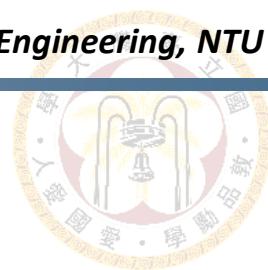

Logically Impossible Path

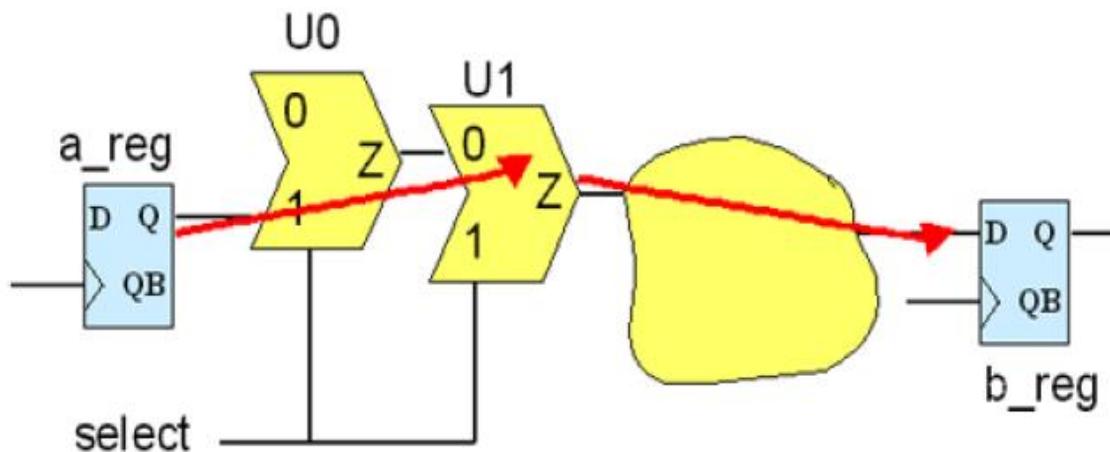
- A path may exist in the circuit but no combination of input vectors may ever exercise it
- PrimeTime attempts to automatically detect "logically impossible false paths" (requires many CPU cycles)
- These situations are quite rare




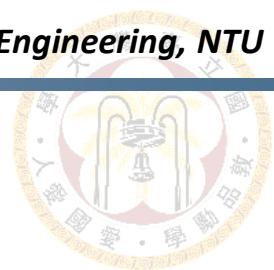

Combinational Loops

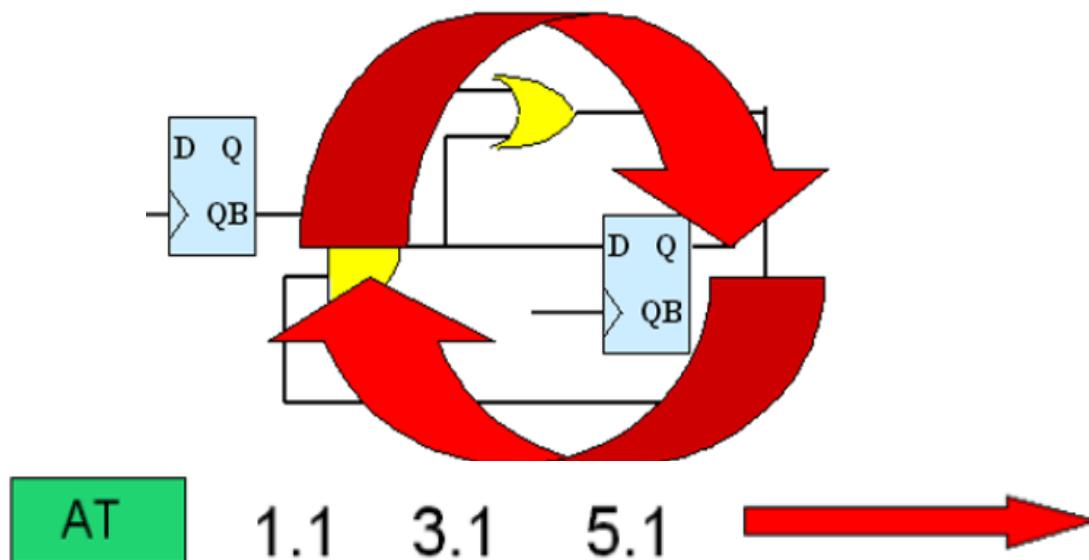
- A combinational loop that needs to be broken
 - Most STA's can't leave combinational loops in the design, as a race condition will occur




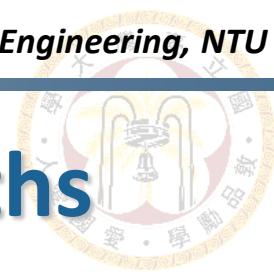


Special Timing Paths: Multicycle Paths

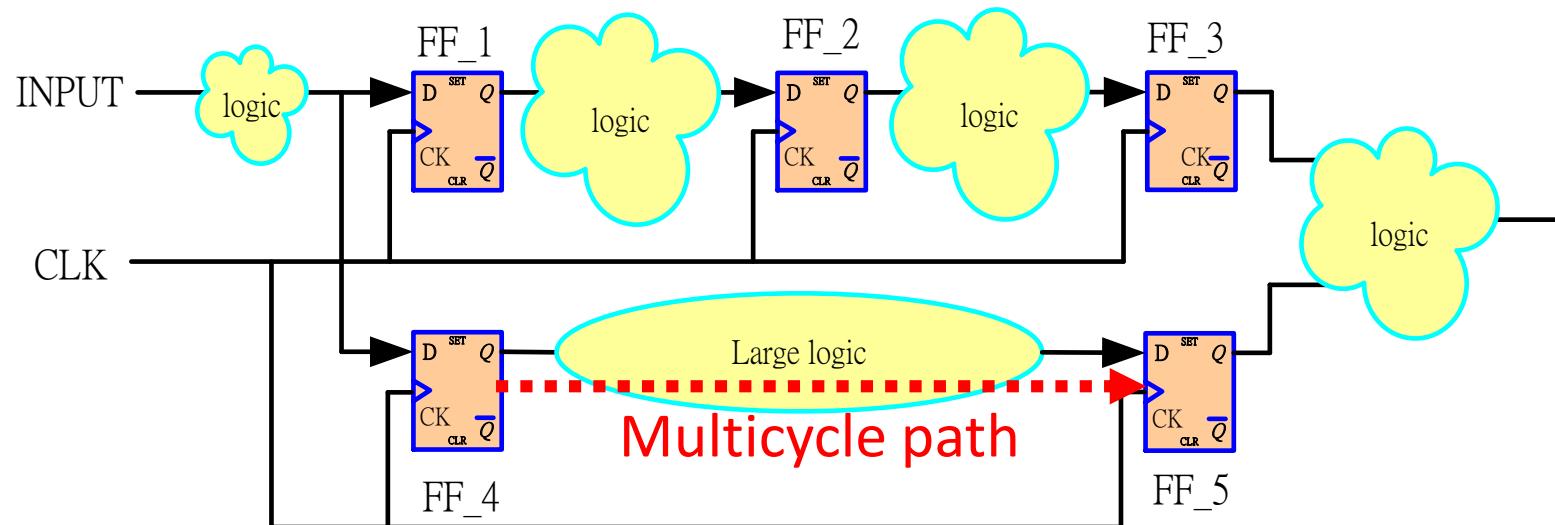- Timing paths that are not expected to propagate signals in one cycle, and are carefully designed so that we can **get the results multiple cycles later**
 - Multiplier/divider



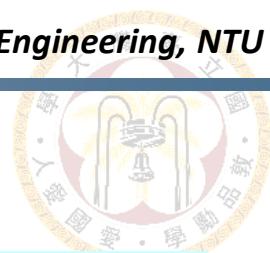

Example: Multiplier

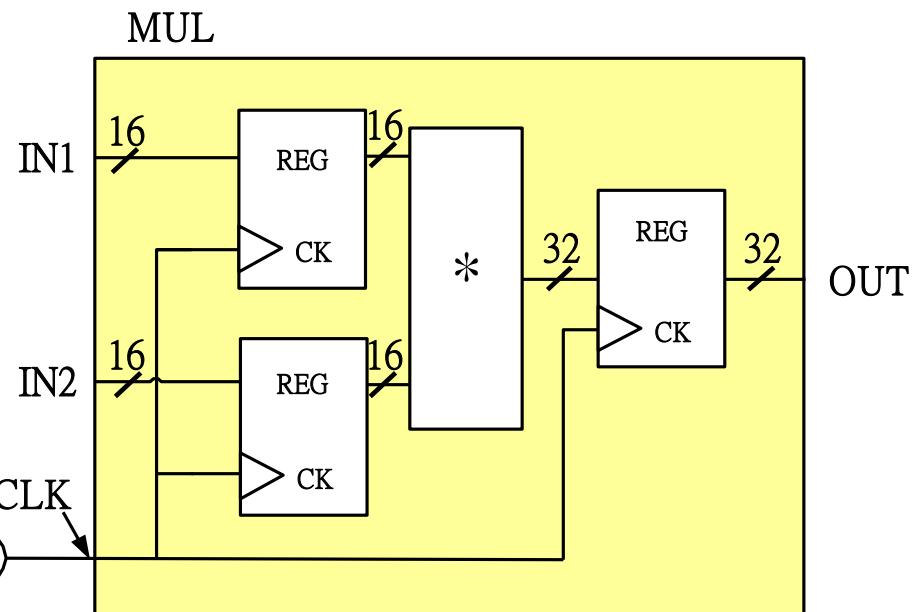

```
module MUL
(
    // Output Port
    OUT,
    // Input Port
    IN1, IN2, CLK
);

output reg[31:0] OUT;
input [15:0] IN1, IN2;
input CLK;


reg [15:0] IN1_R, IN2_R;

always @(posedge CLK)
    IN1_R <= IN1;

always @(posedge CLK)
    IN2_R <= IN2;

always @(posedge CLK)
    OUT <= IN1_R*IN2_R;

endmodule
```

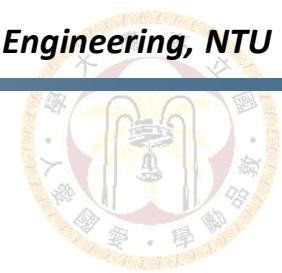


Example: STA Result

```
dc_shell>create_clock -period 4 CLK  
dc_shell>compile  
dc_shell>report_timing
```


Report : timing -path full -delay max -max_paths 1		
Design : MUL		


Point	Incr	Path
clock CLK (rise edge)	0.00	0.00
clock network delay (ideal)	0.00	0.00
IN1_R_reg[14]/CK (DFFHQX4)	0.00	0.00 r
IN1_R_reg[14]/Q (DFFHQX4)	0.30	0.30 r
U14/Y (BUFX20)	0.18	0.48 r
mult_21/A[14]		
(MUL_DW02_mult_16_16_0)	0.00	0.48 r
... (ignored)		
mult_21/PRODUCT[28]		
(MUL_DW02_mult_16_16_0)	0.00	4.91 r
OUT_reg[28]/D (DFFXL)	0.00	4.91 r
data arrival time		4.91
clock CLK (rise edge)	4.00	4.00
clock network delay (ideal)	0.00	4.00
OUT_reg[28]/CK (DFFXL)	0.00	4.00 r
library setup time	-0.10	3.90
data required time		3.90
data required time		3.90
data arrival time		-4.91
slack (VIOLATED)		-1.00

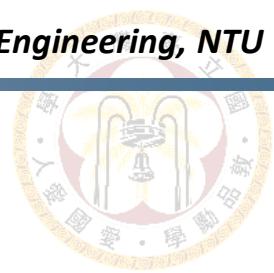

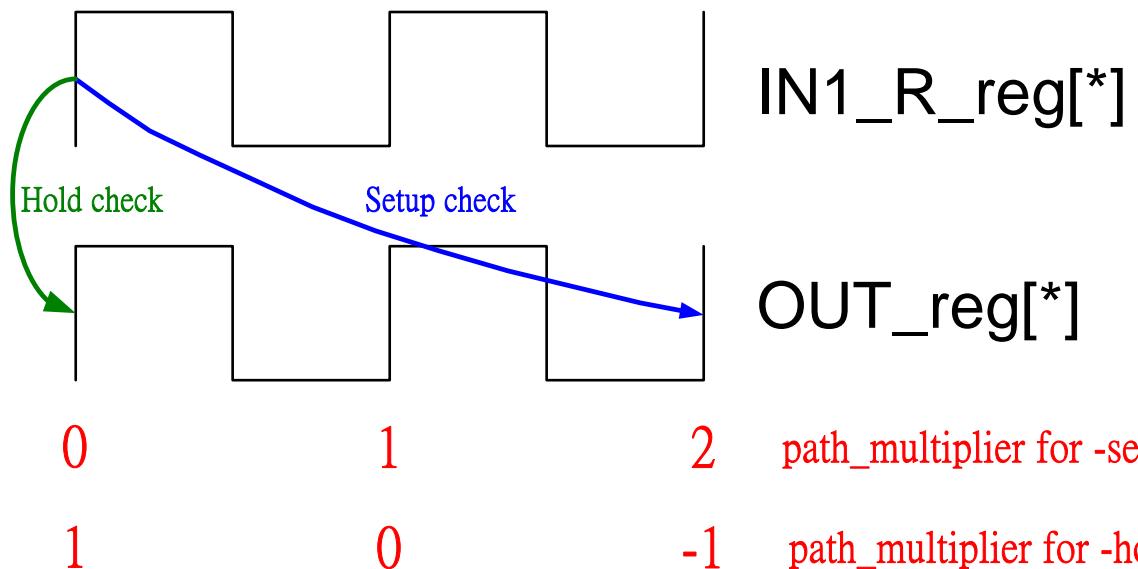Example: Set Multicycle Paths

```
dc_shell>set_multicycle_path 2 -from [get_cells IN1_R_reg[*]] -to [get_cells OUT_reg[*]]  
dc_shell>set_multicycle_path 2 -from [get_cells IN2_R_reg[*]] -to [get_cells OUT_reg[*]]  
dc_shell>set_multicycle_path 1 -hold -end -from [get_cells IN1_R_reg[*]] -to [get_cells OUT_reg[*]]  
dc_shell>set_multicycle_path 1 -hold -end -from [get_cells IN2_R_reg[*]] -to [get_cells OUT_reg[*]]
```



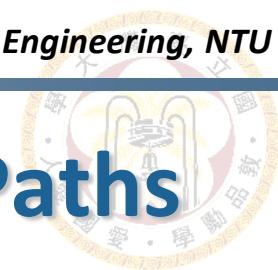

Example: STA Result with Multicycle Paths


```
dc_shell>compile  
dc_shell>report_timing
```

Report : timing -path full -delay max -max_paths 1		
Design : MUL		

Point	Incr	Path
clock CLK (rise edge)	0.00	0.00
clock network delay (ideal)	0.00	0.00
IN1_R_reg[13]/CK (DFFX1)	0.00	0.00 r
IN1_R_reg[13]/Q (DFFX1)	1.27	1.27 r
mult_21/A[13]		
(MUL_DW02_mult_16_16_0)	0.00	1.27 r
.....(ignored)		
mult_21/PRODUCT[28]		
(MUL_DW02_mult_16_16_0)	0.00	7.56 f
OUT_reg[28]/D (DFFX1)	0.00	7.56 f
data arrival time		7.56
clock CLK (rise edge)	8.00	8.00
clock network delay (ideal)	0.00	8.00
OUT_reg[28]/CK (DFFX1)	0.00	8.00 r
library setup time	-0.33	7.67
data required time		7.67


data required time		7.67
data arrival time		-7.56

slack (MET)		0.11

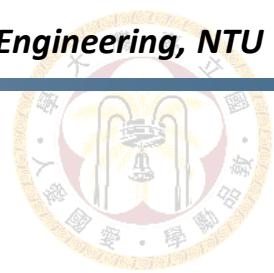


Summary

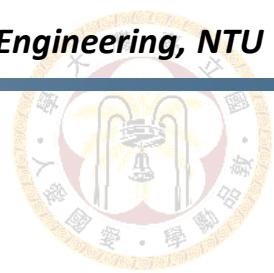- **The importance of timing analysis**
- **DTA vs. STA**
- **Steps of STA**
 - Break the design into timing paths
 - Calculate AT and RT
 - Calculate the slack
- **STA environment**
- **Special timing paths**
 - False path
 - Multicycle path




Supplementary: CDC

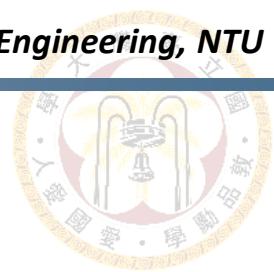
- **Clock domain crossing (CDC) is to transfer data from one clock domain to another clock domain**
- **There are often multiple clock domains in modern designs**
 - Different blocks require different timing constraints
- **Trigger metastability issue**



Supplementary: MetaStability

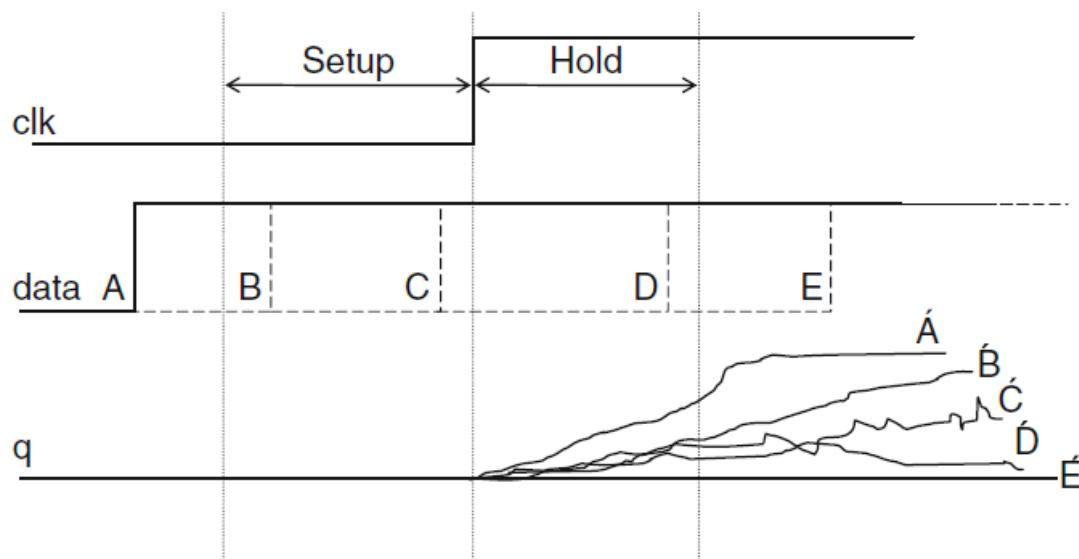
- The unstable status due to non-ideal data transition is called metastability
- To avoid this phenomenon, we have to ensure no data transition during setup/hold timing check




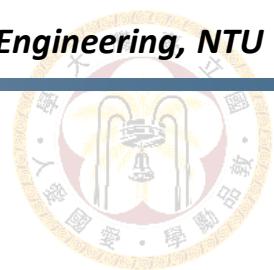



Supplementary: CDC Solution

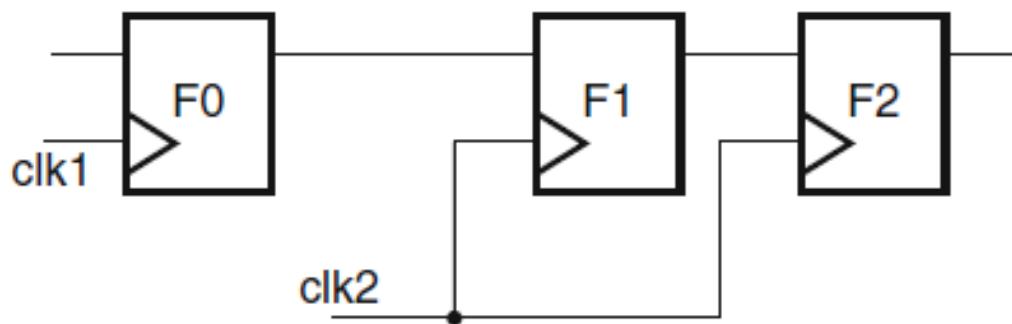
- An easiest way: Double Flop (2-FF) Synchronizer
- F1 samples a CDC signal (probably a meta-stable value)
- F2 captures the F1 output after a full clk2 cycle to permit any metastability
- Often used in 1-bit flag transmission




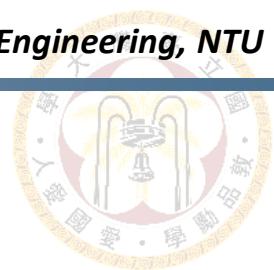



Supplementary: CDC Solution

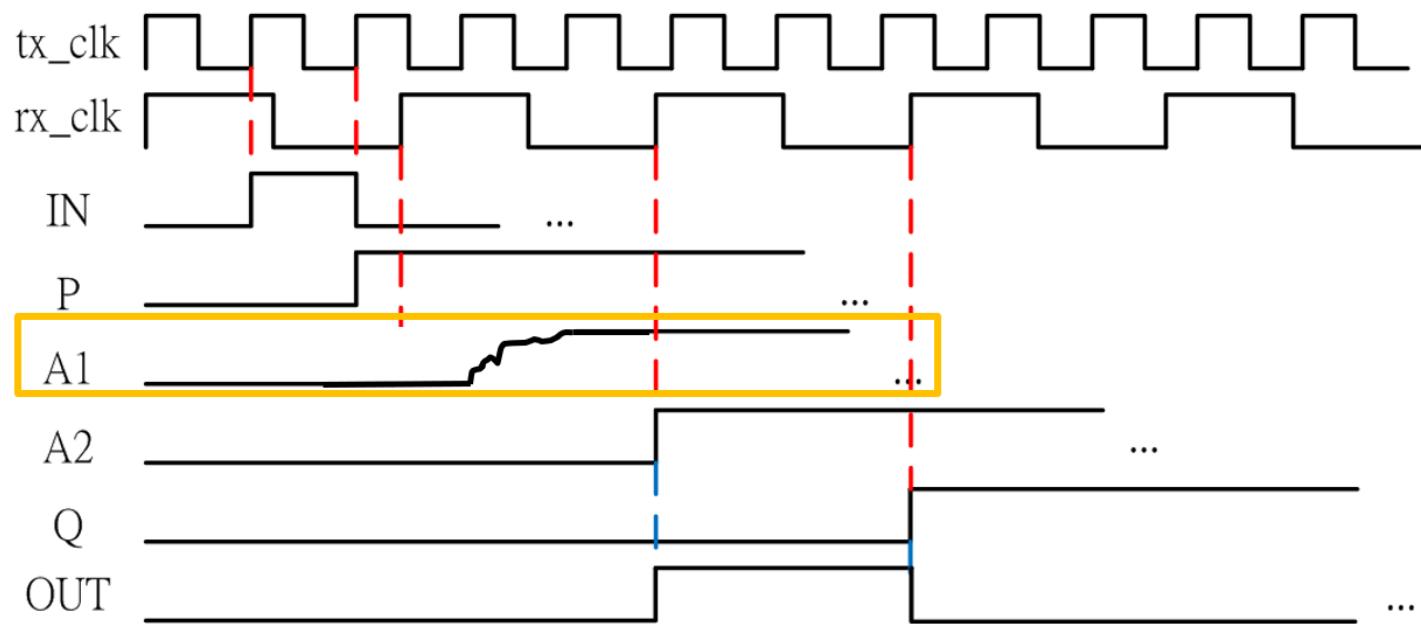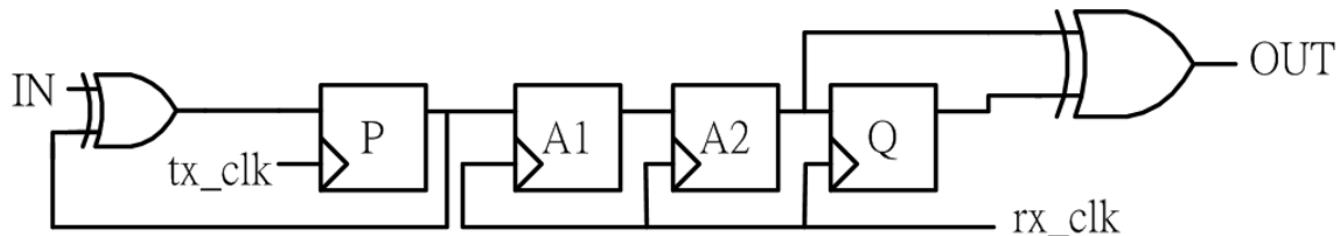

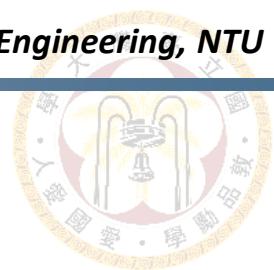

Supplementary: CDC Solution

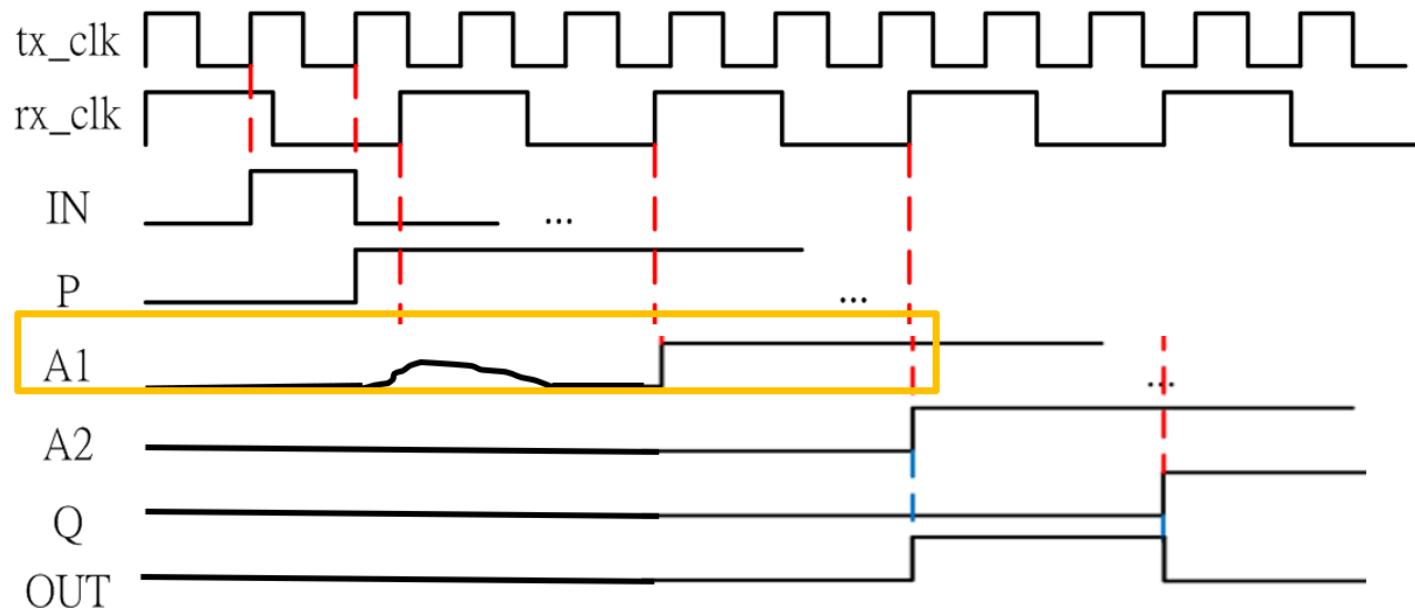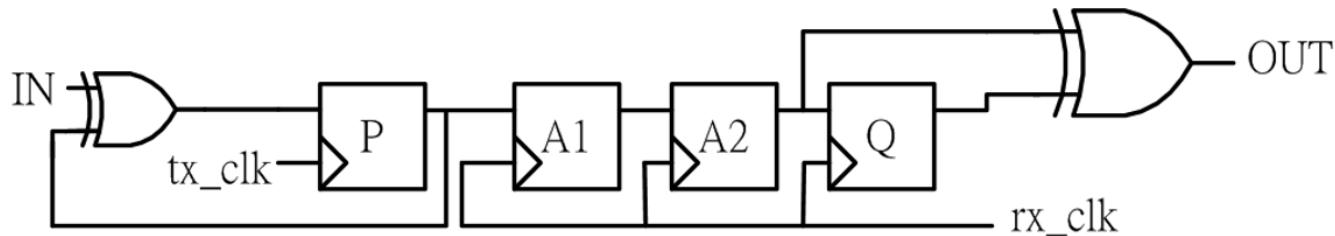

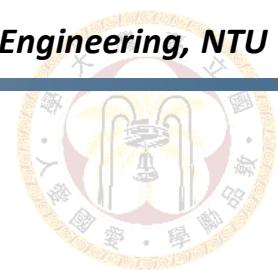

Supplementary: Setup False Path

- Ignore timing constraints from F0 to F1 (CDC boundary)

