

# Computer-Aided VLSI System Design

## Homework 1: Arithmetic Logic Unit

*Graduate Institute of Electronics Engineering, National Taiwan University*



NTU GIEE




## Goal

- In this homework, you will learn
  - How to design ALU with simple operations
  - Differences between combinational circuit and sequential circuit
  - How to define registers and wires
  - How to read spec




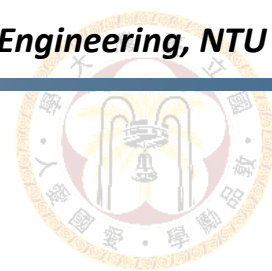
# Introduction

- The Arithmetic logic unit (ALU) is one of the components of a computer processor
- In this homework, you are going to design an ALU with some special instructions, and use the ALU to compute input data to get the correct results




# Block Diagram

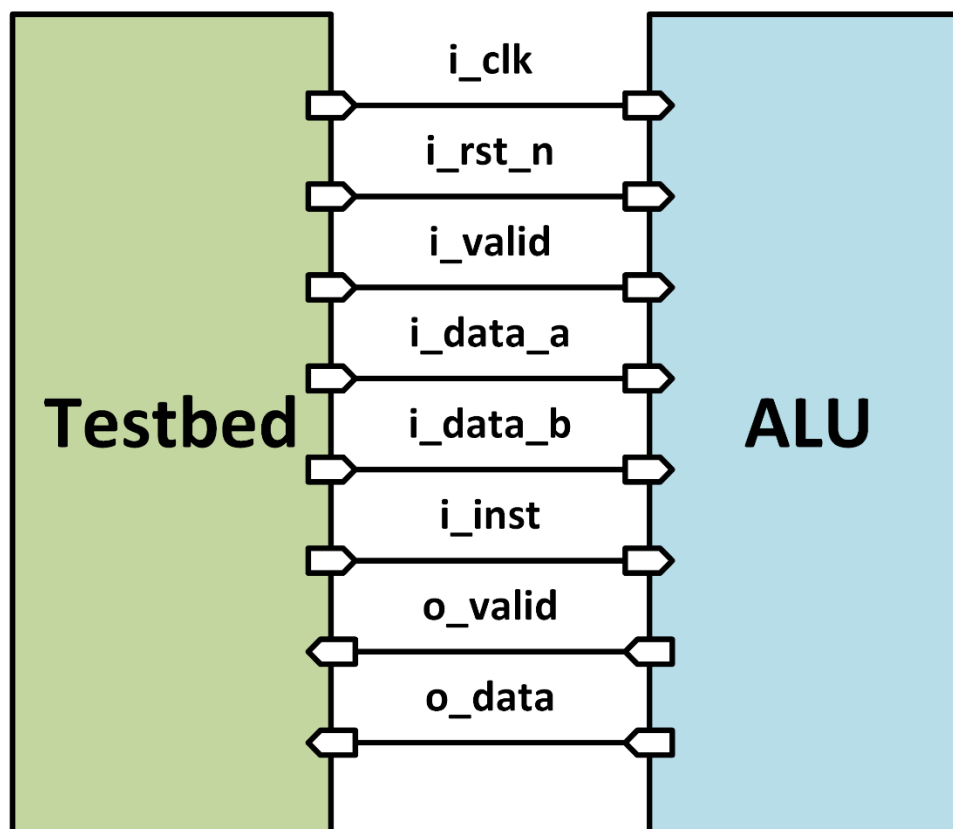

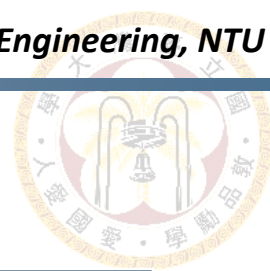


# Input/Output

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system
i_rst_n	I	1	Active <b>low</b> asynchronous reset
i_valid	I	1	The signal is <b>high</b> if input data is ready
i_data_a	I	10	1. For instruction 0000~0100, <b>signed</b> input data with 2's complement representation (4-bit integer + 6-bit fraction) 2. For instruction 0101~1001, no fractional part (10-bit number)
i_data_b	I	10	
i_inst	I	4	Instruction for ALU to operate
o_valid	O	1	Set <b>high</b> if ready to output result
o_data	O	10	1. For instruction 0000~0100, result after ALU processing with 2's complement representation (4-bit integer + 6-bit fraction) 2. For instruction 0101~1001, no fractional part (10-bit number)

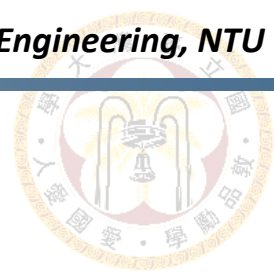
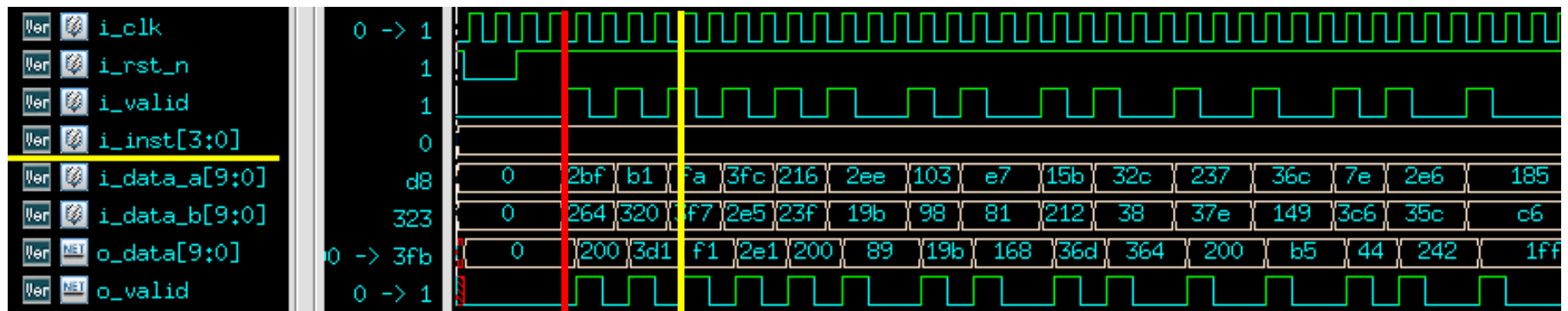
# Specification (1)


- All inputs are synchronized with the negative clock edge
- All outputs should be synchronized at clock **rising** edge (Flip-flops are added before outputs)
- Active low asynchronous reset is used and only once (You should set all your outputs to be zero when i\_rst\_n is **low**)





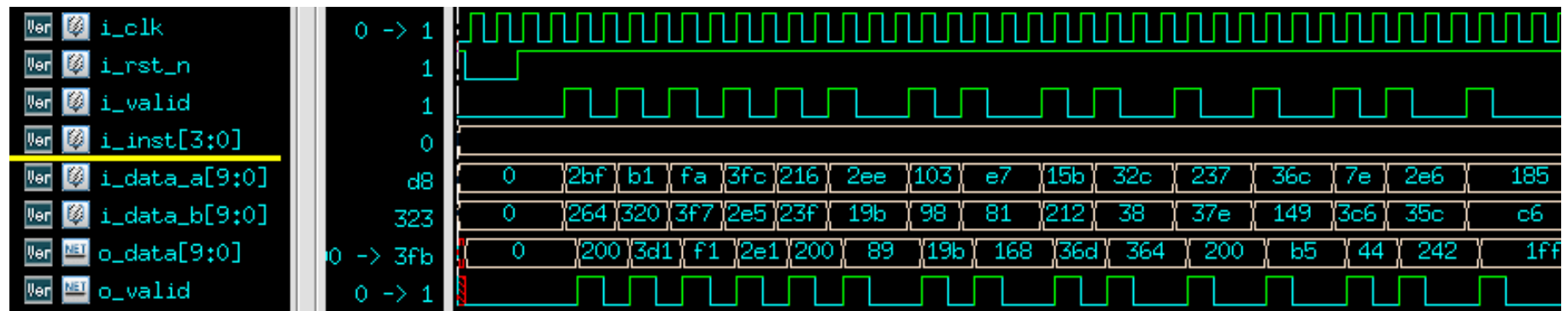
## Specification (2)


- The i\_valid will turn to **high** in one cycle for ALU to get i\_data\_a, i\_data\_b and i\_inst
- The i\_valid will pulled **high** in random
- Your o\_valid should be pulled **high** for only one cycle for every o\_data



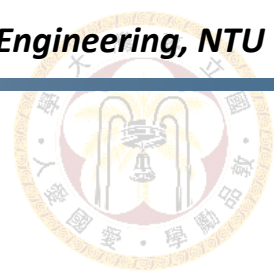

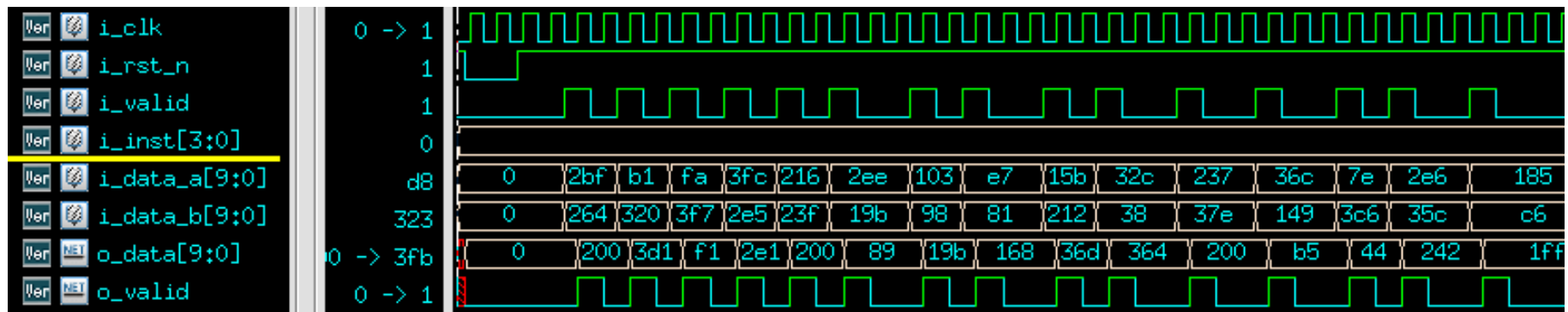
## Specification (3)

- The testbed will get your output at negative clock edge to check the answer when your o\_valid is **high**
- You can raise your o\_valid at any moment.





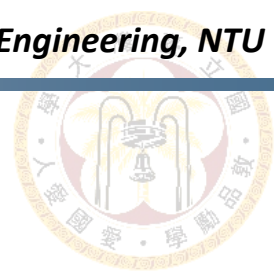

# Instruction

Operation	i_inst [3:0]	Meaning	Note
Signed Addition	4'b0000	$o\_data = i\_data\_a + i\_data\_b$	Overflow may be happened
Signed Subtraction	4'b0001	$o\_data = i\_data\_a - i\_data\_b$	
Signed Multiplication	4'b0010	$o\_data = i\_data\_a * i\_data\_b$	
MAC	4'b0011	$o\_mult = i\_data\_a * i\_data\_b$ $o\_data_{new} = o\_mult + o\_data_{old}$	
Tanh	4'b0100	$o\_data = \tanh(i\_data\_a)$	Piecewise linear approximation
ORN	4'b0101	$o\_data = i\_data\_a   i\_data\_b'$	Bit-wise operation
CLZ	4'b0110	Count leading zero bits	Only i_data_a is used
CTZ	4'b0111	Count trailing zero bits	
CPOP	4'b1000	Count set bits	
ROL	4'b1001	Rotate left	View i_data_b as shift amount




# Output Saturation & Rounding

- For instructions 0000, 0001, 0010, and 0011, If the output value exceeds the maximum value of 10-bit representation, use the maximum value as output, and vice versa
- For instructions 0010, 0011 and 0100, the result needs to be **rounded to the nearest number**
  - Check reference [3]


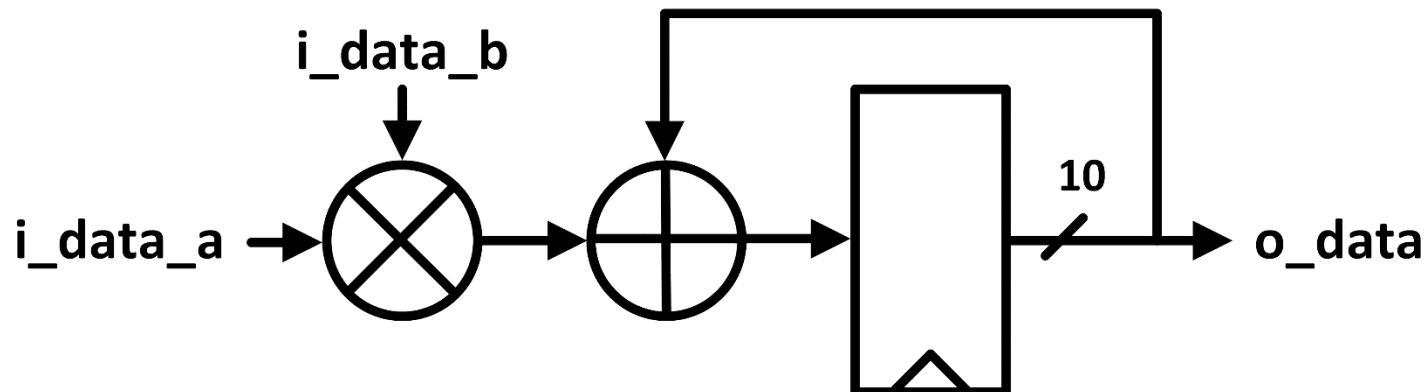
# MAC


- For instruction 0011, you have to implement Multiply–accumulate operation (MAC) function
- The output of the Flip-flop must be rounded to the nearest number




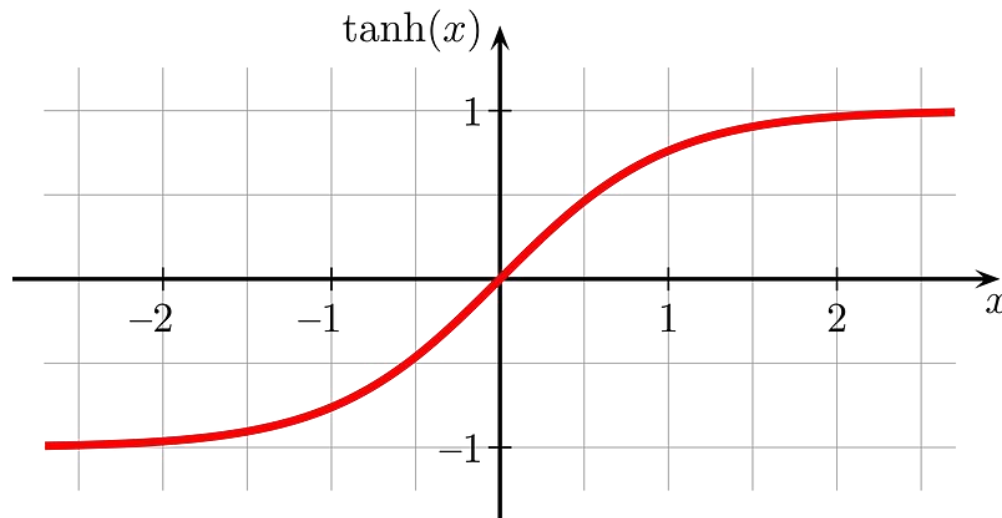
# Tanh Function

- For instruction 0100, you need to implement a popular activation function, a hyperbolic tangent function. It becomes preferred over the sigmoid function as it gives better performance for multi-layer neural networks
- However, it's not intuitive to implement an exponential operation on hardware




$$\tanh(x) = \frac{2}{1 + e^{-2x}} - 1$$


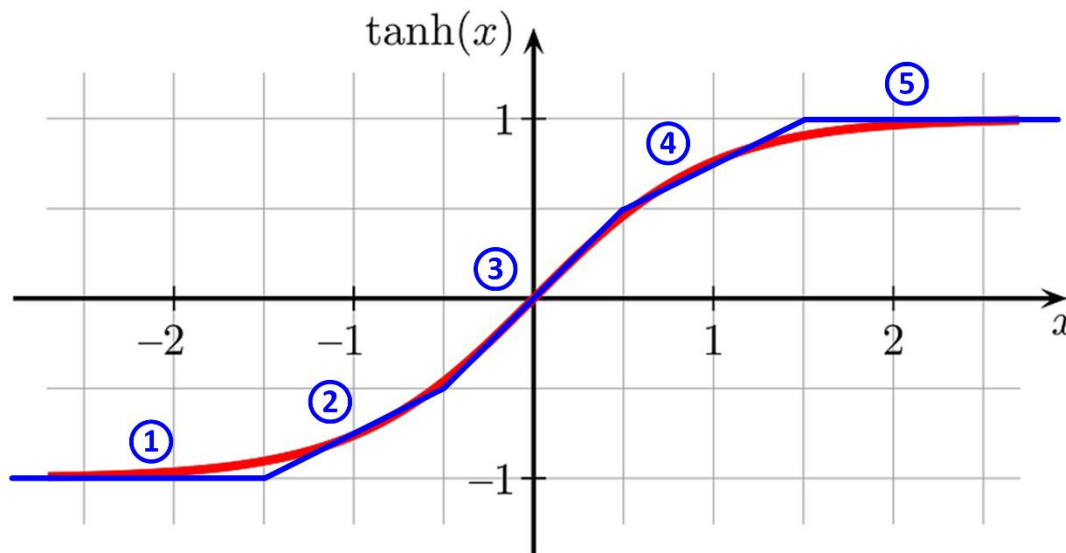
# Tanh Function Approximation


- In order to simplify the implementation, we use **piecewise linear approximation** to compute tanh function
- We divide the curve into **5 segments** to compute the output




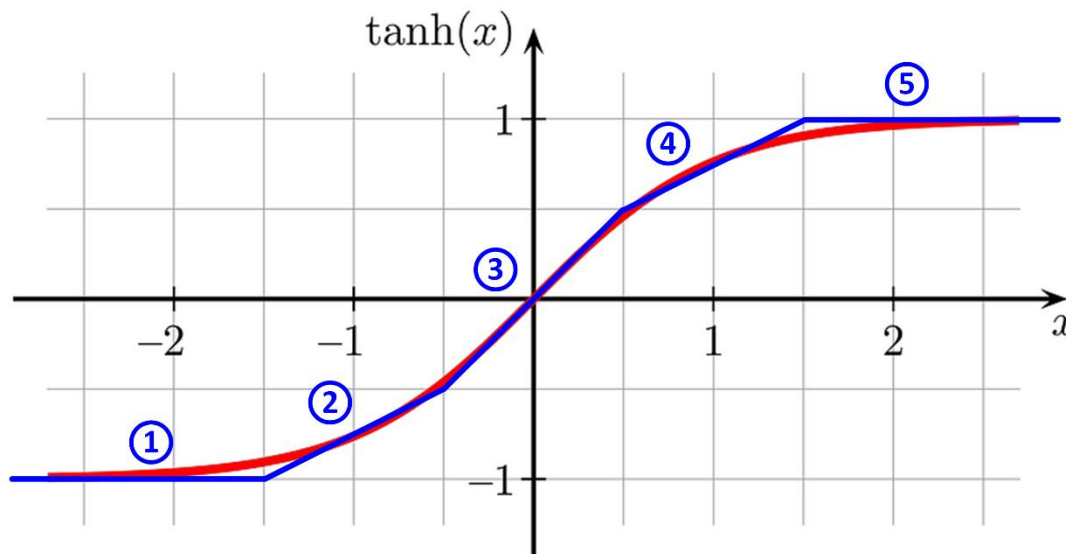
# Tanh Function Approximation

- Choose the slope of the 2<sup>nd</sup>, 3<sup>rd</sup>, 4<sup>th</sup> segment appropriately
- The 5 segments have 4 intersections
  - $(-1.5, -1)$ ,  $(-0.5, -0.5)$ ,  $(0.5, 0.5)$ ,  $(1.5, 1)$
- Output must be **rounded to the nearest number**





## CLZ

- For instruction 0110, count leading zero
  - Count the number of zero bits from MSB end
- For example, if  $a = 8'b0010\_0000$ , then  $CLZ(a)=2$

0010\_0000  
MSB →




## CTZ

- For instruction 0111, count trailing zero
  - Count the number of zero bits from LSB end
- For example, if  $a = 8'b0010\_0000$ , then  $CTZ(a)=5$

0010\_0000\_


← LSB



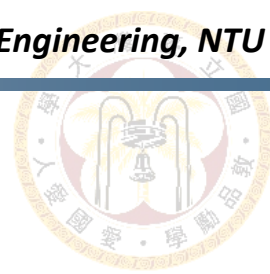
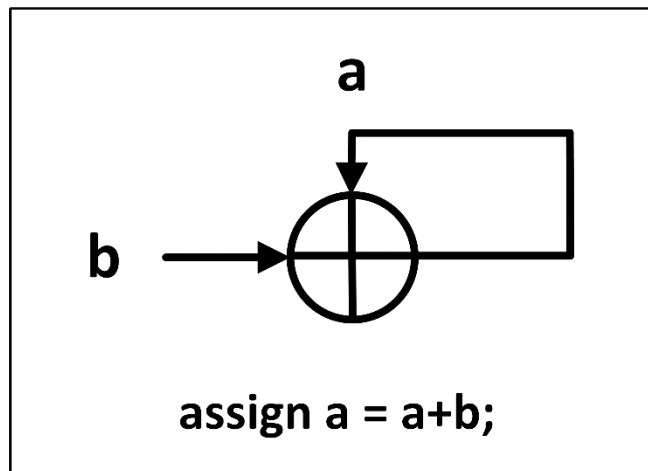
## CPOP

- For instruction 1000, count the number of set bits
- For example, if  $a = 8'b0010\_0001$ , then  $CPOP(a)=2$
- Note you have to **avoid** the **combinational loop**, where static timing analysis (STA) cannot be applied




An error example



 
# ROL

- For instruction 1001, you need to implement **rotate left** and view `i_data_b` as the **rotation amount**
  - The range of `i_data_b`: 0~9
- In rotation, the shifted bits will be filled into the vacant position



Left rotate 1 bit

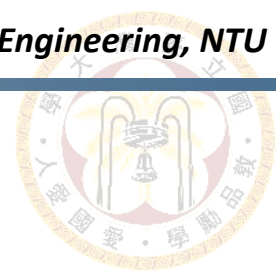

# alu.v

```
module alu #(
    parameter INT_W  = 4,
    parameter FRAC_W = 6,
    parameter INST_W = 4,
    parameter DATA_W = INT_W + FRAC_W
)(
    input                i_clk,
    input                i_rst_n,
    input                i_valid,
    input signed [DATA_W-1:0] i_data_a,
    input signed [DATA_W-1:0] i_data_b,
    input               [INST_W-1:0] i_inst,
    output              o_valid,
    output [DATA_W-1:0] o_data
); // Do not modify

// -----
// Wires and Registers
// -----
reg [DATA_W-1:0] o_data_w, o_data_r;
reg              o_valid_w, o_valid_r;
// ---- Add your own wires and registers here if needed ---- //
```




# alu.v

```
// -----  
// Continuous Assignment  
// -----  
assign o_valid = o_valid_r;  
assign o_data = o_data_r;  
// ---- Add your own wire data assignments here if needed ---- //  
  
// -----  
// Combinational Blocks  
// -----  
// ---- Write your combinational block design here ---- //  
always@(*) begin  
    o_data_w = ;  
    o_valid_w = ;  
end
```


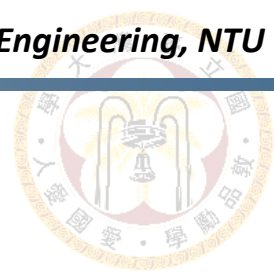
# alu.v

```
// -----  
// Sequential Block  
// -----  
// ---- Write your sequential block design here ---- //  
always@(posedge i_clk or negedge i_rst_n) begin  
    if (!i_rst_n) begin  
        o_data_r <= 0;  
        o_valid_r <= 0;  
    end else begin  
        o_data_r <= o_data_w;  
        o_valid_r <= o_valid_w;  
    end  
end  
  
endmodule
```



# testbench.v

```

`timescale 1ns/1ps
`define CYCLE      10.0
`define RST_DELAY  2
`define MAX_CYCLE  100000

`ifdef I0
  `define Inst_I  "../00_TESTBED/pattern/INST0_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST0_O.dat"
  `define PAT_NUM 40
`elsif I1
  `define Inst_I  "../00_TESTBED/pattern/INST1_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST1_O.dat"
  `define PAT_NUM 40
`elsif I2
  `define Inst_I  "../00_TESTBED/pattern/INST2_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST2_O.dat"
  `define PAT_NUM 40
`elsif I3
  `define Inst_I  "../00_TESTBED/pattern/INST3_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST3_O.dat"
  `define PAT_NUM 40
`elsif I4
  `define Inst_I  "../00_TESTBED/pattern/INST4_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST4_O.dat"
  `define PAT_NUM 40

```

```

`elsif I5
  `define Inst_I  "../00_TESTBED/pattern/INST5_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST5_O.dat"
  `define PAT_NUM 40
`elsif I6
  `define Inst_I  "../00_TESTBED/pattern/INST6_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST6_O.dat"
  `define PAT_NUM 40
`elsif I7
  `define Inst_I  "../00_TESTBED/pattern/INST7_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST7_O.dat"
  `define PAT_NUM 40
`elsif I8
  `define Inst_I  "../00_TESTBED/pattern/INST8_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST8_O.dat"
  `define PAT_NUM 40
`elsif I9
  `define Inst_I  "../00_TESTBED/pattern/INST9_I.dat"
  `define Inst_O  "../00_TESTBED/pattern/INST9_O.dat"
  `define PAT_NUM 40
`endif

```



# Commands

- ./01\_run arg1

```
ncverilog -f rtl.f +define+<arg1> +access+rw
```

– For example:

```
./01_run I0
```

- ./99\_clean


```
rm -rf *.history *.key *.log
```

```
rm -rf novas.rc novas.fsdb novas.conf
```

```
rm -rf INCA_libs nWaveLog BSSLib.lib++
```

- Note before you execute the shell script, change the permission of the file by


```
chmod +x 01_run
```

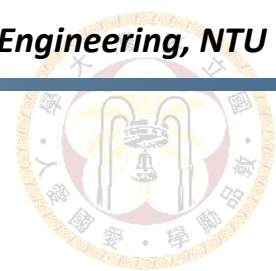

## Pattern (Input Data)

i_inst	i_data_a	i_data_b
0000	110100111001	000100010101
0000	1010010000	1110011101
0000	0000110011	0101010100
0000	1011111001	101111000
0000	1000101011	0011100010
0000	0011010101	1101111101
0000	1011101001	0100001000



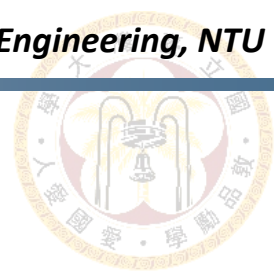

# Pattern (Golden Output)

**o\_data**

```
0001100011
1000101101
0110000111
1001110100
1100001101
0001010010
1111110001
0001111110
```



# Grading Policy (1)

- Released pattern **70%**
  - I0~I4: 40%
  - I5~I9: 30%
- Hidden pattern: **30%**
  - Hidden pattern contains all instructions
    - I0~I4: 10000
    - I5~I9: 10000
  - Only if you pass all patterns will you get the full 30% score



## Grading Policy (2)

- No late submission
  - **0 point** for this homework
- Lose **3 points** for any wrong naming rule or format for submission
- No plagiarize




# Submission

- Create a folder named **studentID\_hw1** and follow the hierarchy below

```
r11943123_hw1/  
├── 01_RTL  
│   ├── alu.v  
│   └── rtl.f
```

 - Compress the folder **studentID\_hw1** in a tar file named **studentID\_hw1\_vk.tar** ( $k$  is the number of version,  $k = 1, 2, \dots$ )
  - Note: Use lower case in your student ID.  
(Ex. r11943123\_hw1\_v1.tar)
- Submit to NTU Cool



# Discussion

☰ 電腦輔助積體電路系統設計 (EEE5022) > 討論 > [HW1]Discussion

111-2

首頁

課程資訊

課程內容

公告

作業

成績

討論

文件

頁面

成員

線上測驗

設定

## [HW1]Discussion

所有班別

**HW1**相關問題在此討論，並請以下列格式發問，方便助教按照每個問題回答

1. 問題一

2. 問題二

...

另外，若需要截圖，請勿把自己的code截圖或code文字上傳，變成大家的參考答案，若違反將扣本次作業總分10分。

[提醒]

1. ...

2. ...

3. ...

祝同學們學習順心

TA



## References

- [1] Reference for 2's complement:
  - [https://en.wikipedia.org/wiki/Two%27s\\_complement](https://en.wikipedia.org/wiki/Two%27s_complement)
- [2] Reference for fixed-point representation
  - [Fixed-Point Representation: The Q Format and Addition Examples](#)
- [3] Reference for rounding to the nearest:
  - [Rounding - MATLAB & Simulink \(mathworks.com\)](#)